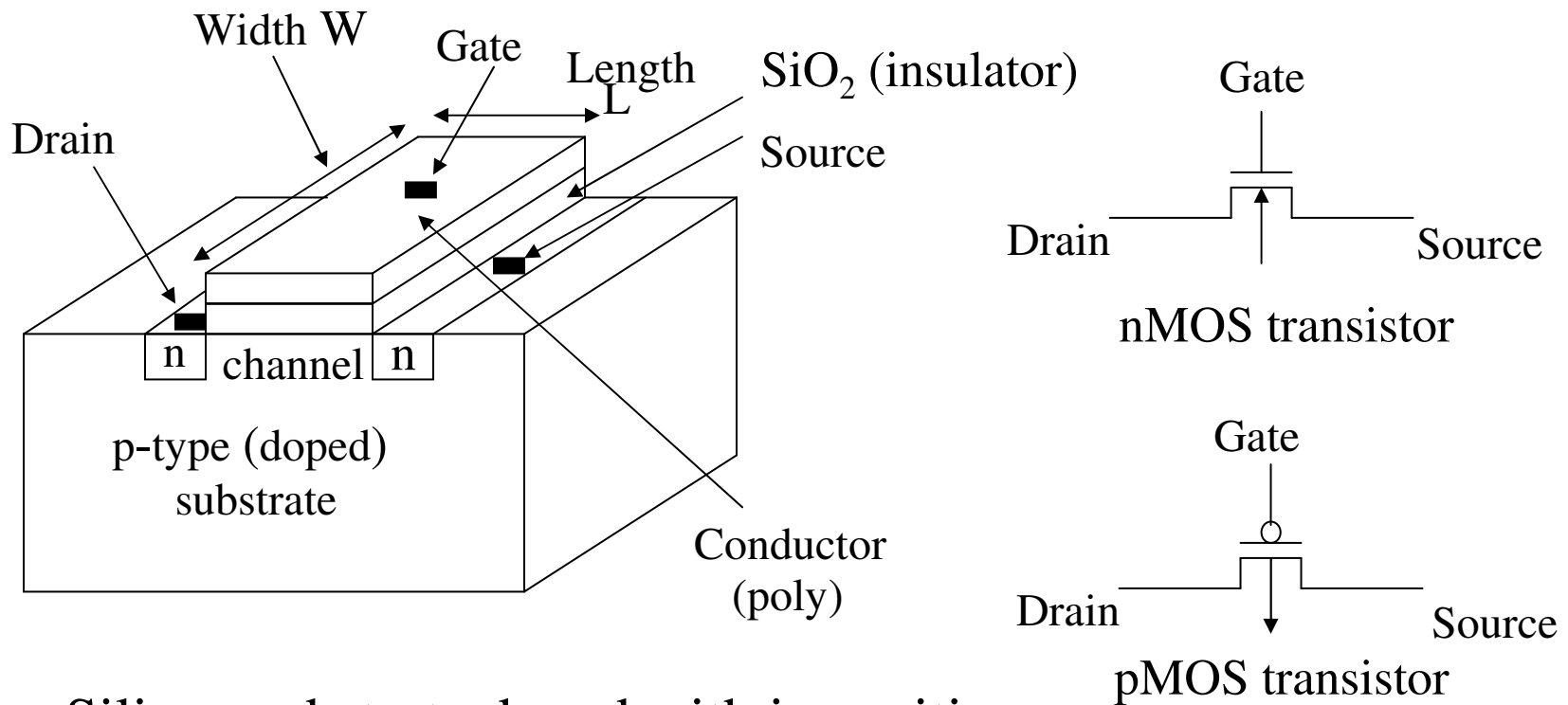



MOS Transistors



- Silicon substrate doped with impurities
- Adding or cutting away insulating glass (SiO_2)
- Adding wires made of polycrystalline silicon (*polysilicon*, *poly*) or metal, insulated from the substrate by SiO_2


Silicon Lattice

 - Transistors are built on a silicon substrate
- Silicon is a Group IV material
- Forms crystal lattice with bonds to four neighbors




Dopants

 - Silicon is a semiconductor
- Pure silicon has no free carriers and conducts poorly
- Adding dopants increases the conductivity
- Group V: extra electron (n-type)
- Group III: missing electron, called hole (p-type)




p-n Junctions

 - A junction between p-type and n-type semiconductor forms a diode.
- Current flows only in one direction




anode

cathode

 


nMOS Transistor

 - Four terminals: gate, source, drain, body
- Gate – oxide – body stack looks like a capacitor
 - Gate and body are conductors
 - SiO_2 (oxide) is a very good insulator
 - Called metal – oxide – semiconductor (MOS) capacitor
 - Even though gate is no longer made of metal




nMOS Operation

 - Body is commonly tied to ground (0 V)
- When the gate is at a low voltage:
 - P-type body is at low voltage
 - Source-body and drain-body diodes are OFF
 - No current flows, transistor is OFF




nMOS Operation Cont.

 - When the gate is at a high voltage:
 - Positive charge on gate of MOS capacitor
 - Negative charge attracted to body
 - Inverts a channel under gate to n-type
 - Now current can flow through n-type silicon from source through channel to drain, transistor is ON



pMOS Transistor

 - Similar, but doping and voltages reversed
 - Body tied to high voltage (V_{DD})
 - Gate low: transistor ON
 - Gate high: transistor OFF
 - Bubble indicates inverted behavior




Power Supply Voltage

- $\text{GND} = 0 \text{ V}$
- In 1980's, $V_{\text{DD}} = 5\text{V}$
- V_{DD} has decreased in modern processes
 - High V_{DD} would damage modern tiny transistors
 - Lower V_{DD} saves power
- $V_{\text{DD}} = 3.3, 2.5, 1.8, 1.5, 1.2, 1.0, \dots$







Transistors as Switches

 - We can view MOS transistors as electrically controlled switches
- Voltage at gate controls path from source to drain



MOS Transistor Switches







N-switch

      

Good 0, Poor 1






MOS Transistor Switches

P-switch

      

Good 1, Poor 0

CMOS switch
(Transmission gate)

    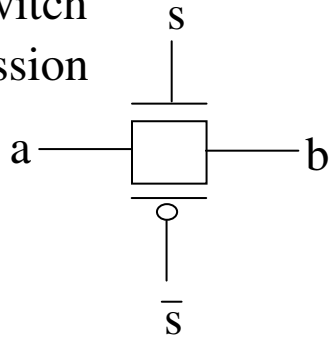



Good 0
Good 1

Signal Strength

- *Strength* of signal
 - How close it approximates ideal voltage source
- V_{DD} and GND rails are strongest 1 and 0
- nMOS pass strong 0
 - But degraded or weak 1
- pMOS pass strong 1
 - But degraded or weak 0
- Thus nMOS are best for pull-down network


CMOS Inverter

A	Y
0	
1	

  


CMOS Logic Gates-1

Inverter

 

2-input NAND

 

Pull-down truth table

a	b	z
0	0	Z
0	1	Z
1	0	Z
1	1	0

Pull-up truth table



a	b	z
0	0	1
0	1	1
1	0	1
1	1	Z

NAND truth table

a	b	z
0	0	1
0	1	1
1	0	1
1	1	0



CMOS Inverter

A	Y
0	
1	0

  



CMOS Inverter

A	Y
0	1
1	0

  



CMOS NAND Gate

A	B	Y
0	0	
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	

  



CMOS NAND Gate

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

  


CMOS NOR Gate

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

  

CMOS Logic Gates-2

2-input NOR

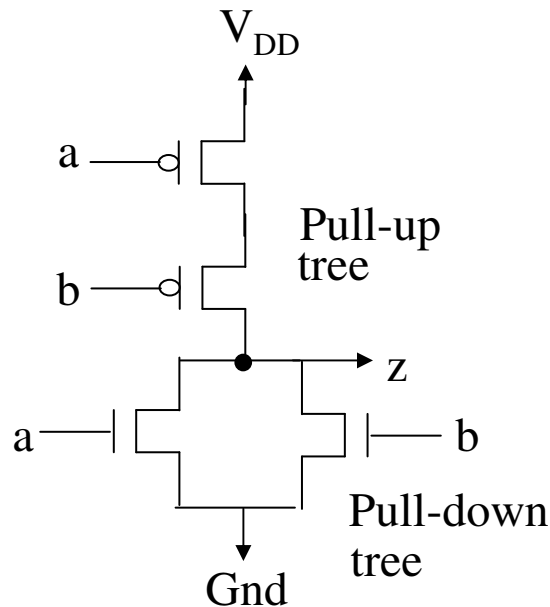

Pull-down truth table		
a	b	z
0	0	Z
0	1	0
1	0	0
1	1	0

Pull-up truth table		
a	b	z
0	0	1
0	1	Z
1	0	Z
1	1	Z

NOR truth table		
a	b	z
0	0	1
0	1	0
1	0	0
1	1	0


- There is always (for all input combinations) a path from *either* 1 or 0 to the output
- No direct path from 1 to 0 (low power dissipation)
- *Fully restored* logic
- No ratio-ing is necessary (*ratio-less* logic)
- Generalize to n-input NAND and n-input NOR?

3-input NAND Gate


- Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0

3-input NAND Gate

 - Y pulls low if ALL inputs are 1
- Y pulls high if ANY input is 0



CMOS Compound (Complex) Gates-1

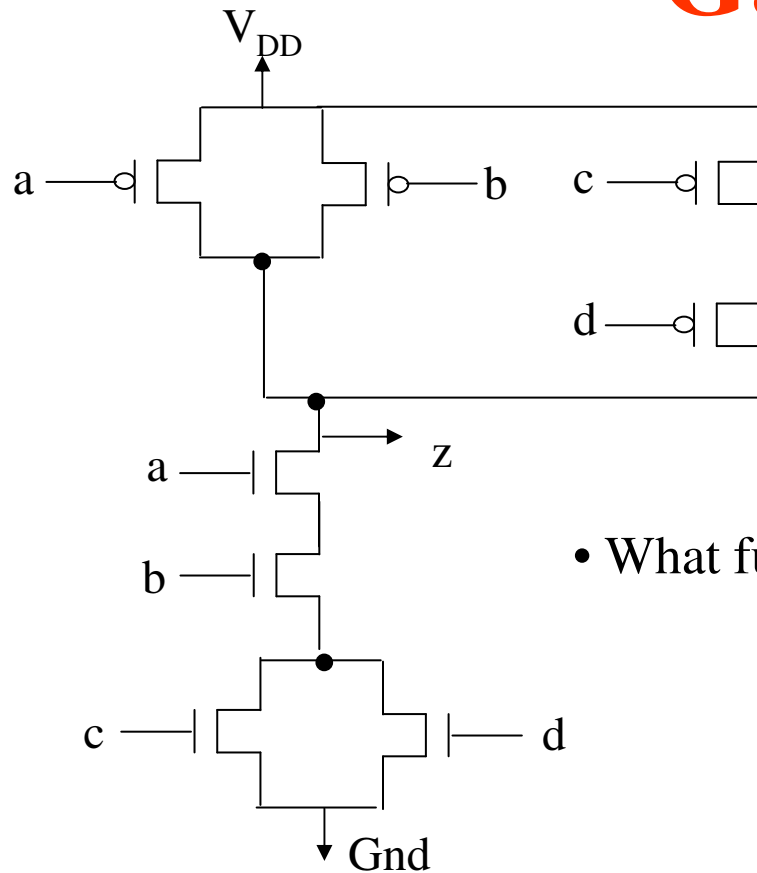


- What function is implemented by this circuit?



Compound Gates-2

How to implement
 $F = ab + bc + ca$?



- $F = ab + bc + ca$

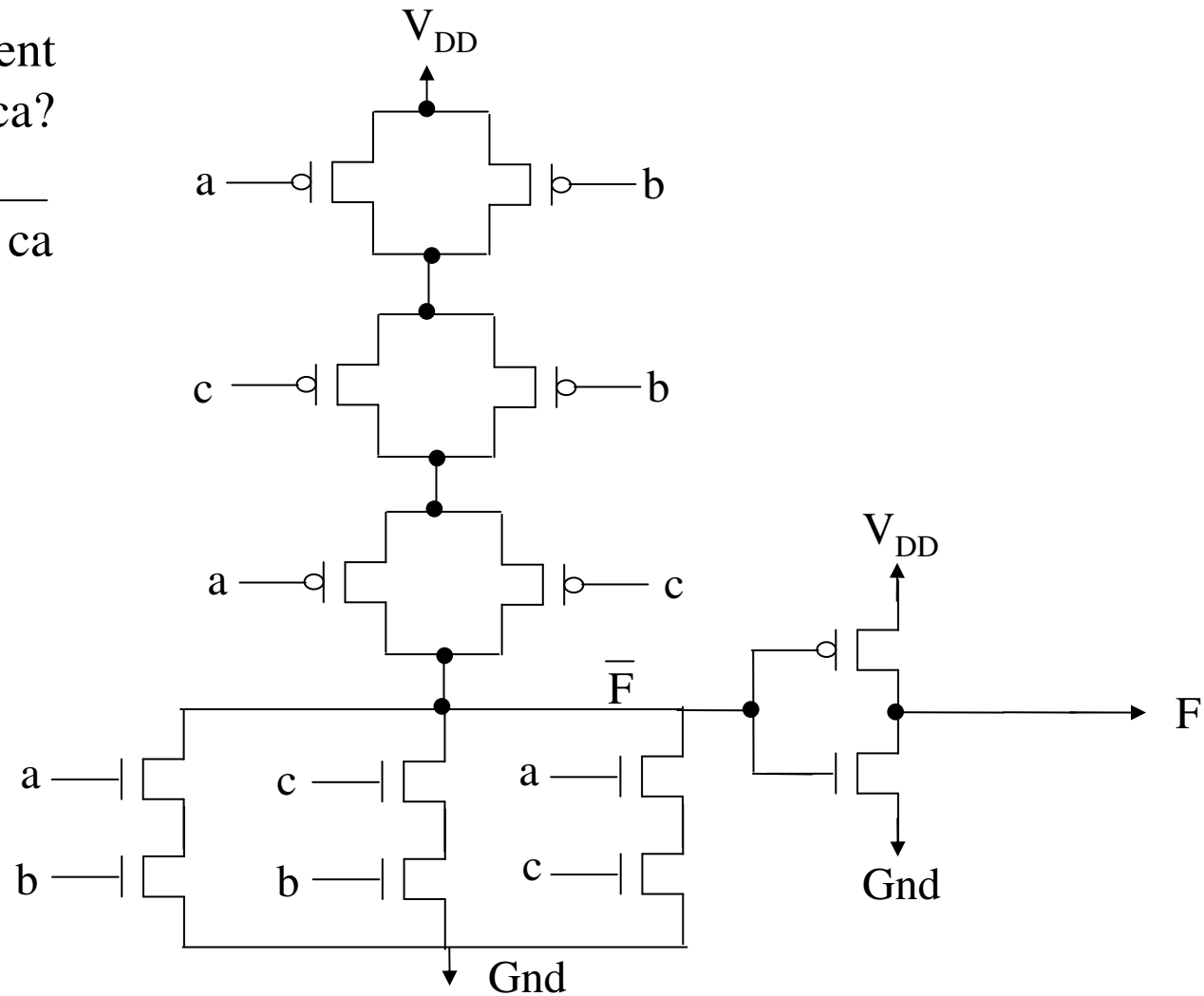

And-Or-Invert (AOI) Gates

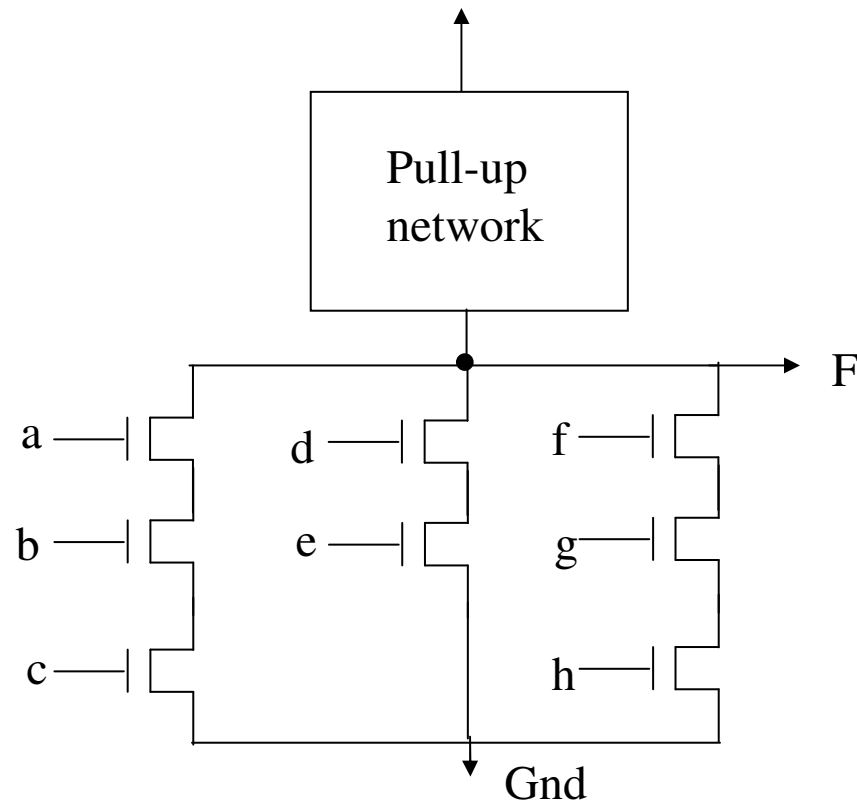 

Or-And-Invert (OAI) Gate

  


- Generally, complex CMOS gates can be derived directly from maxterms of the function (as in a Karnaugh map)

Transmission Gates

- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well

Transmission Gates


 
- Pass transistors produce degraded outputs
- *Transmission gates* pass both 0 and 1 well



Tristates

- *Tristate buffer* produces Z when not enabled



EN	A	Y
0	0	
0	1	
1	0	
1	1	

  

Tristates


- *Tristate buffer* produces Z when not enabled

EN	A	Y
0	0	Z
0	1	Z
1	0	0
1	1	1

  


Nonrestoring Tristate

 - Transmission gate acts as tristate buffer
 - Only two transistors
 - But *nonrestoring*
 - Noise on A is passed on to Y




Tristate Inverter

 - Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Tristate Inverter

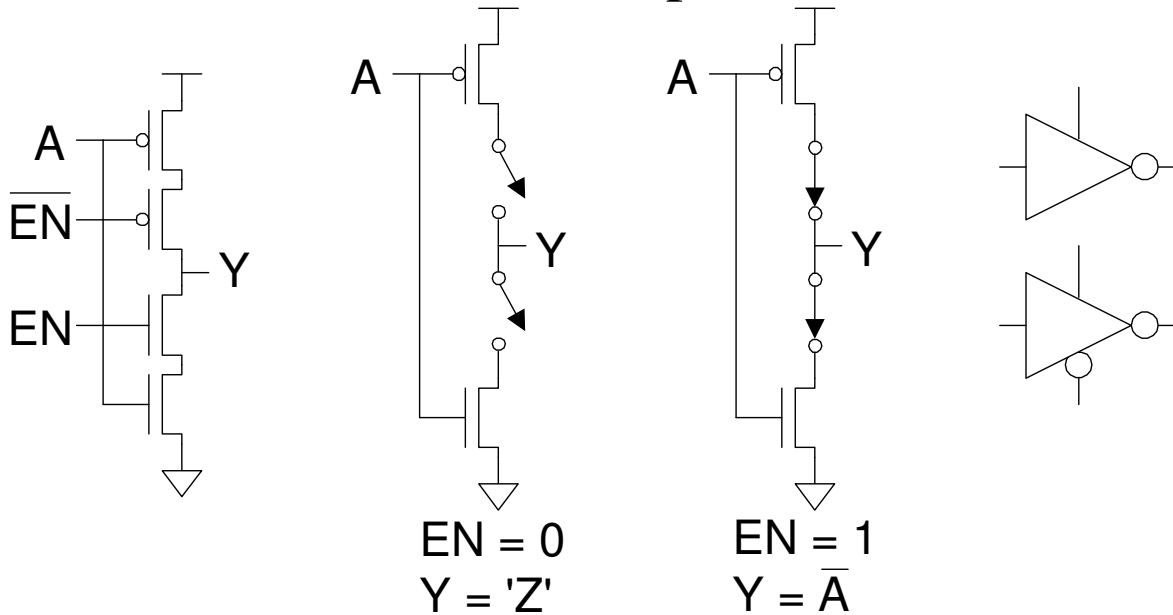
- Tristate inverter produces restored output
 - Violates conduction complement rule
 - Because we want a Z output



Multiplexers

- *2:1 multiplexer* chooses between two inputs


S	D1	D0	Y
0	X	0	
0	X	1	
1	0	X	
1	1	X	

 

Multiplexers

- 2:1 multiplexer chooses between two inputs

S	D1	D0	Y
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1

 

Gate-Level Mux Design



$$Y = SD_1 + \bar{S}D_0 \text{ (too many transistors)}$$

- How many transistors are needed?

Gate-Level Mux Design

$$Y = SD_1 + \bar{S}D_0 \text{ (too many transistors)}$$

- How many transistors are needed? 20

  


Transmission Gate Mux

- Nonrestoring mux uses two transmission gates


Transmission Gate Mux

 - Nonrestoring mux uses two transmission gates
 - Only 4 transistors



Inverting Mux

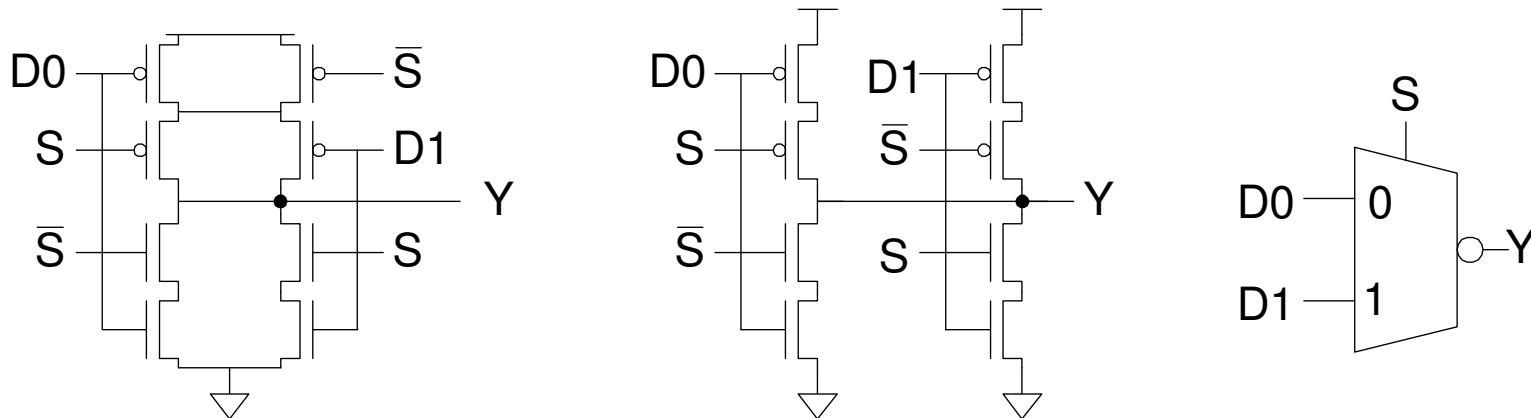- Inverting multiplexer
 - Use compound AOI22
 - Or pair of tristate inverters
 - Essentially the same thing
- Noninverting multiplexer adds an inverter





4:1 Multiplexer

- 4:1 mux chooses one of 4 inputs using two selects


4:1 Multiplexer

  - 4:1 mux chooses one of 4 inputs using two selects
 - Two levels of 2:1 muxes
 - Or four tristates



CMOS Exclusive-Nor Gate

- 8-transistor implementation

 


a	b	TG ₁	TG ₂	F
0	0	nonconducting	conducting	\overline{B} (1)
0	1	nonconducting	conducting	\overline{B} (0)
1	0	conducting	nonconducting	B (0)
1	1	conducting	nonconducting	B (1)

- Better, 6-transistor implementation is possible!



D Latch

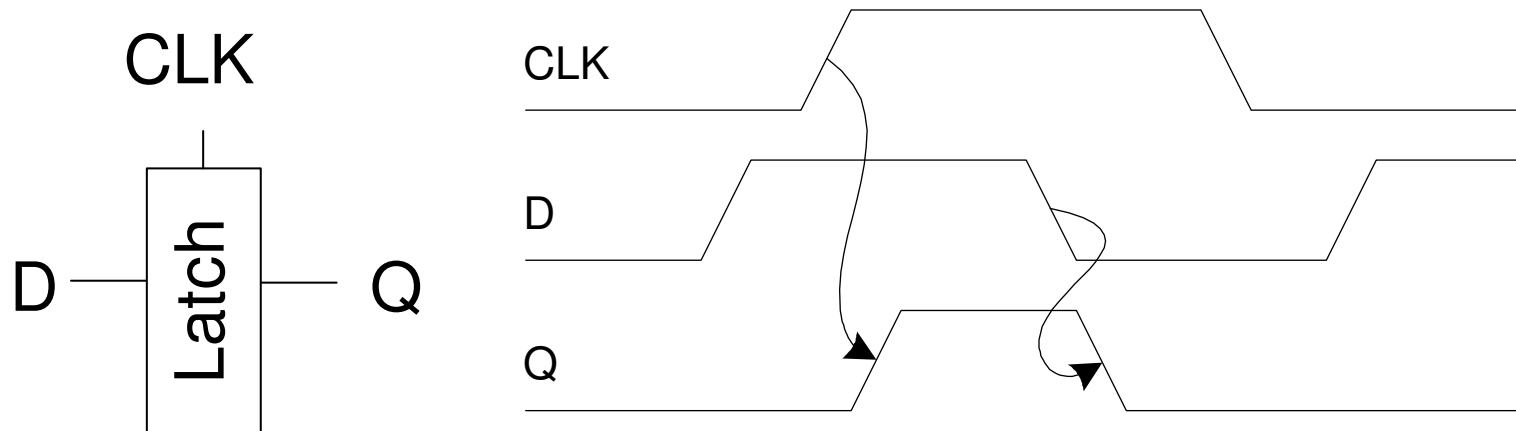- When $CLK = 1$, latch is *transparent*
 - D flows through to Q like a buffer
- When $CLK = 0$, the latch is *opaque*
 - Q holds its old value independent of D
- a.k.a. *transparent latch* or *level-sensitive latch*





D Latch Design

- Multiplexer chooses D or old Q

  


D Latch Operation

 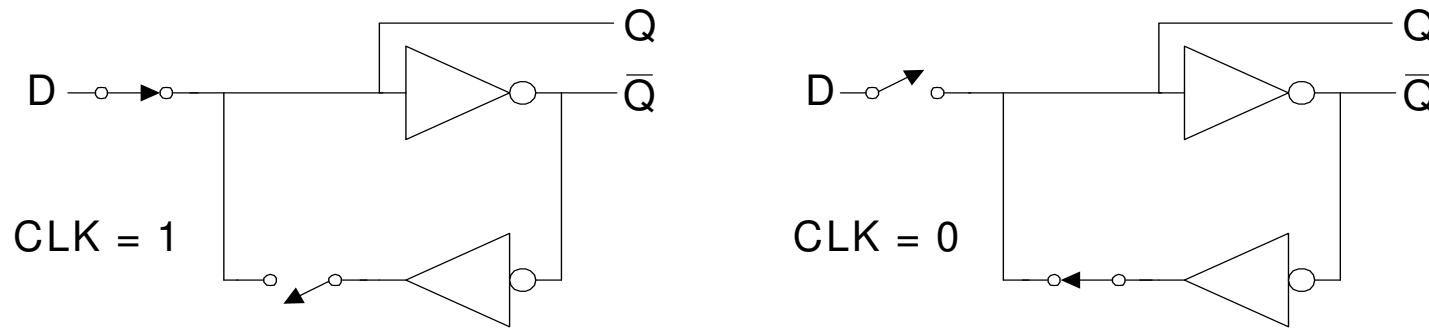


D Flip-flop

 - When CLK rises, D is copied to Q
- At all other times, Q holds its value
- a.k.a. *positive edge-triggered flip-flop, master-slave flip-flop*




D Flip-flop Design

- Built from master and slave D latches

 


D Flip-flop Operation

 


Race Condition

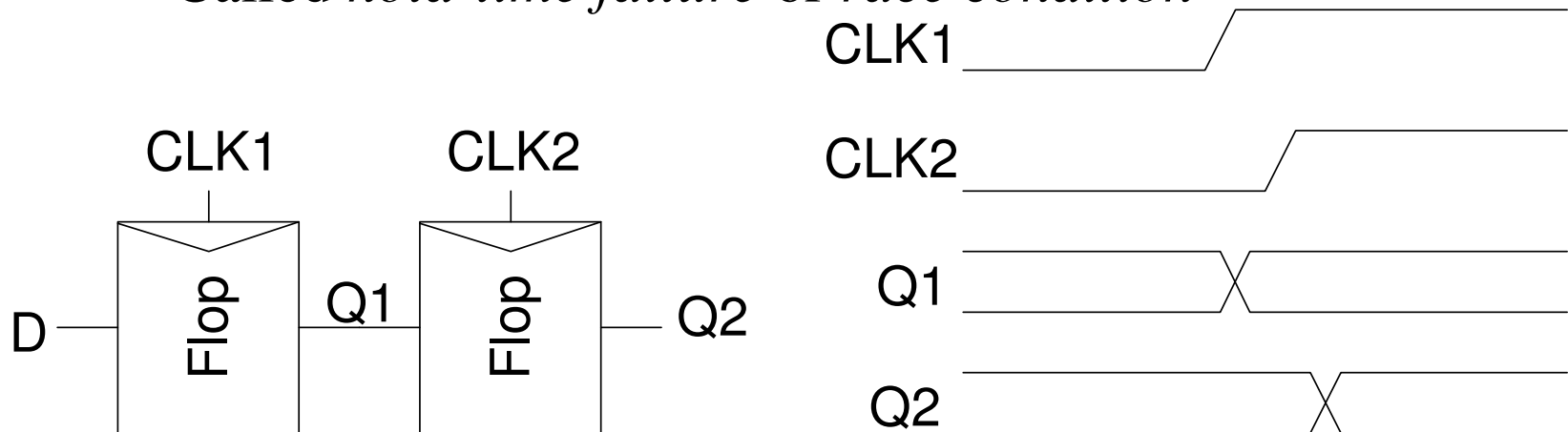- Back-to-back flops can malfunction from clock skew
 - Second flip-flop fires late
 - Sees first flip-flop change and captures its result
 - Called *hold-time failure* or *race condition*



Nonoverlapping Clocks

 - Nonoverlapping clocks can prevent races
 - As long as nonoverlap exceeds clock skew
- We will use them in this class for safe design
 - Industry manages skew more carefully instead




Design Representation Levels

- Design domains

- Behavioral
- Structural
- Physical

 Gajski and Kuhn's Y-chart
(layered like an onion)



- Hardware description languages commonly used at behavioral level, e.g. VHDL, Verilog

- Example: Consider the carry function $c_0 = ab + bc + c_1a$

Verilog Example (Behavioral)

Boolean equation form:

```
module carry (co, a, b, ci);  
output co;  
input a, b, ci;  
assign  
    co = (a & b) | (a & ci) | (b & ci);  
end module
```

Timing information:

```
module carry (co, a, b, ci);  
output co;  
input a, b, ci;  
Wire #10 co = (a & b) | (a & ci) | (b & ci);  
end module
```

c_o changes 10 time units after a, b, or c changes

Boolean truth table form:


```
primitive carry (co, a, b, ci);  
output co;  
input a, b, ci;  
table  
    // a  b  c  co  
    1  1  ?  : 1;  
    1  ?  1  : 1;  
    ?  1  1  : 1;  
    0  0  ?  : 0;  
    0  ?  0  : 0;  
    ?  0  0  : 0;  
end table  
end module
```

Verilog Example (Structural)

Structural representation of 4-bit adder (top-down) :

```
module add4 (s, c4, ci, a, b);  
  output [3:0] s;  
  output [3:0] c4;  
  input [3:0] a, b;  
  input ci;  
  wire [2:0] co;  
  add a0 (co[0], s[0], a[0], b[0], ci);  
  add a1 (co[1], ..., b[1], co[0]);  
  add a2 (co[2], ..., co[1]);  
  add a3 (c4, s[3], a[3], b[3], co[2]);  
end module
```

3-bit
internal
signal

 

```
module add (co, s, a, b, ci);  
  output s, co;  
  input a, b, ci;  
  sum s1 (s, a, b, ci);  
  carry c1 (co, a, b, ci);  
end module
```



```
module carry (co, a, b, ci);  
  output co;  
  input a, b, ci;  
  wire x, y, z;  
  and g1 (y, z, b);  
  and g2 (z, b, ci);  
  and g3 (z, a, ci);  
  or g4 (co, x, y, z);  
end module
```

Technology-independent