

Performance Characterization


- Delay analysis
- Transistor sizing
- Logical effort
- Power analysis

Delay Definitions

- t_{pdr} : *rising propagation delay*
 - From input to rising output crossing $V_{DD}/2$
- t_{pdf} : *falling propagation delay*
 - From input to falling output crossing $V_{DD}/2$
- t_{pd} : *average propagation delay*
 - $t_{pd} = (t_{pdr} + t_{pdf})/2$
- t_r : *rise time*
 - From output crossing $0.2 V_{DD}$ to $0.8 V_{DD}$
- t_f : *fall time*
 - From output crossing $0.8 V_{DD}$ to $0.2 V_{DD}$

Simulated Inverter Delay

 - Solving differential equations by hand is too hard
- SPICE simulator solves the equations numerically
 - Uses more accurate I-V models too!
- But simulations take time to write




Delay Estimation

- We would like to be able to easily estimate delay
 - Not as accurate as simulation
 - But easier to ask “What if?”
- The step response usually looks like a 1st order RC response with a decaying exponential.
- Use RC delay models to estimate delay
 - C = total capacitance on output node
 - Use *effective resistance* R
 - So that $t_{pd} = RC$
- Characterize transistors by finding their effective R
 - Depends on average current as gate switches

RC Delay Models

 - Use equivalent circuits for MOS transistors
 - Ideal switch + capacitance and ON resistance
 - Unit nMOS has resistance R , capacitance C
 - Unit pMOS has resistance $2R$, capacitance C
- Capacitance proportional to width
- Resistance inversely proportional to width




Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).

 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).



 
Example: 3-input NAND

- Sketch a 3-input NAND with transistor widths chosen to achieve effective rise and fall resistances equal to a unit inverter (R).




3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




3-input NAND Caps

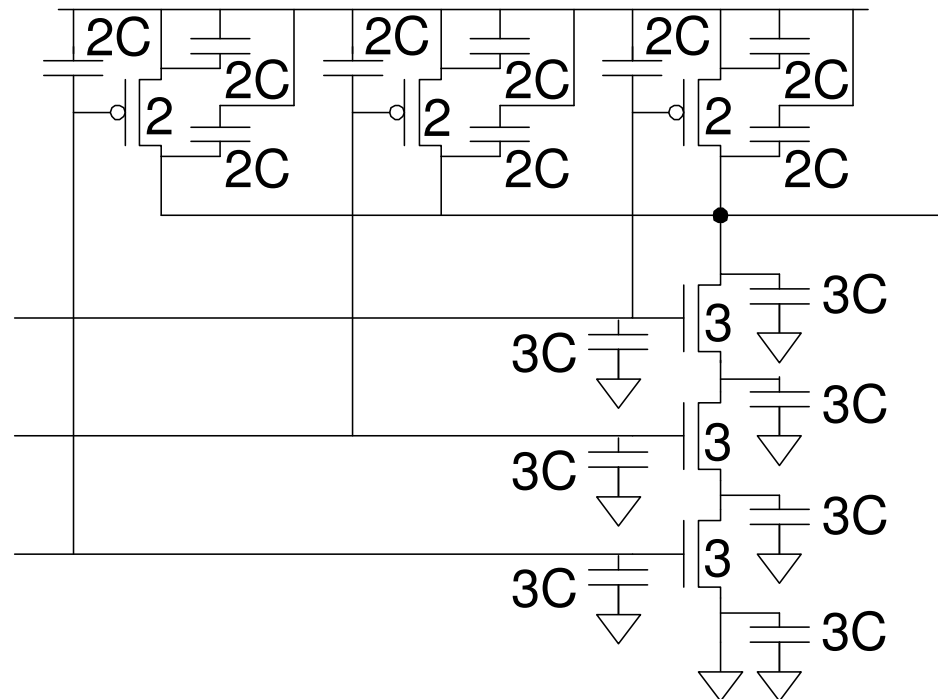- Annotate the 3-input NAND gate with gate and diffusion capacitance.



3-input NAND Caps

 - Annotate the 3-input NAND gate with gate and diffusion capacitance.




Elmore Delay

- ON transistors look like resistors
- Pullup or pulldown network modeled as *RC ladder*
- Elmore delay of RC ladder


$$t_{pd} \approx \sum_{\text{nodes } i} R_{i\text{-to-source}} C_i$$
 
$$= R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + R_2 + \dots + R_N) C_N$$



 
Example: 2-input NAND

- Estimate worst-case rising and falling delay of 2-input NAND driving h identical gates.





 
Example: 2-input NAND

- Estimate rising and falling propagation delays of a 2-input NAND driving h identical gates.



  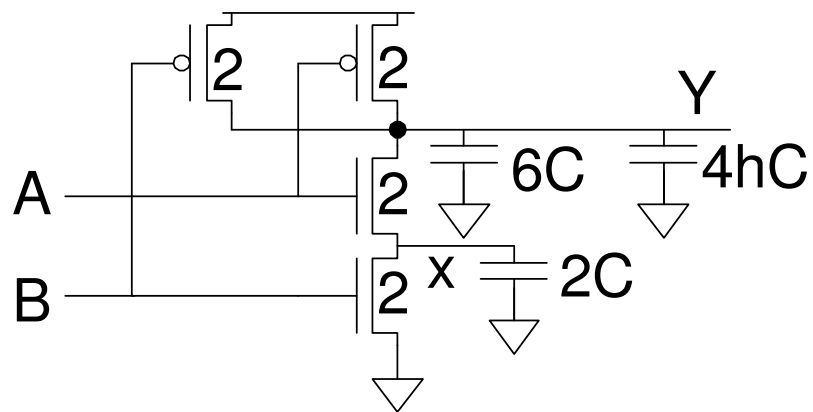
Example: 2-input NAND

- Estimate **rising** and falling propagation delays of a 2-input NAND driving h identical gates.




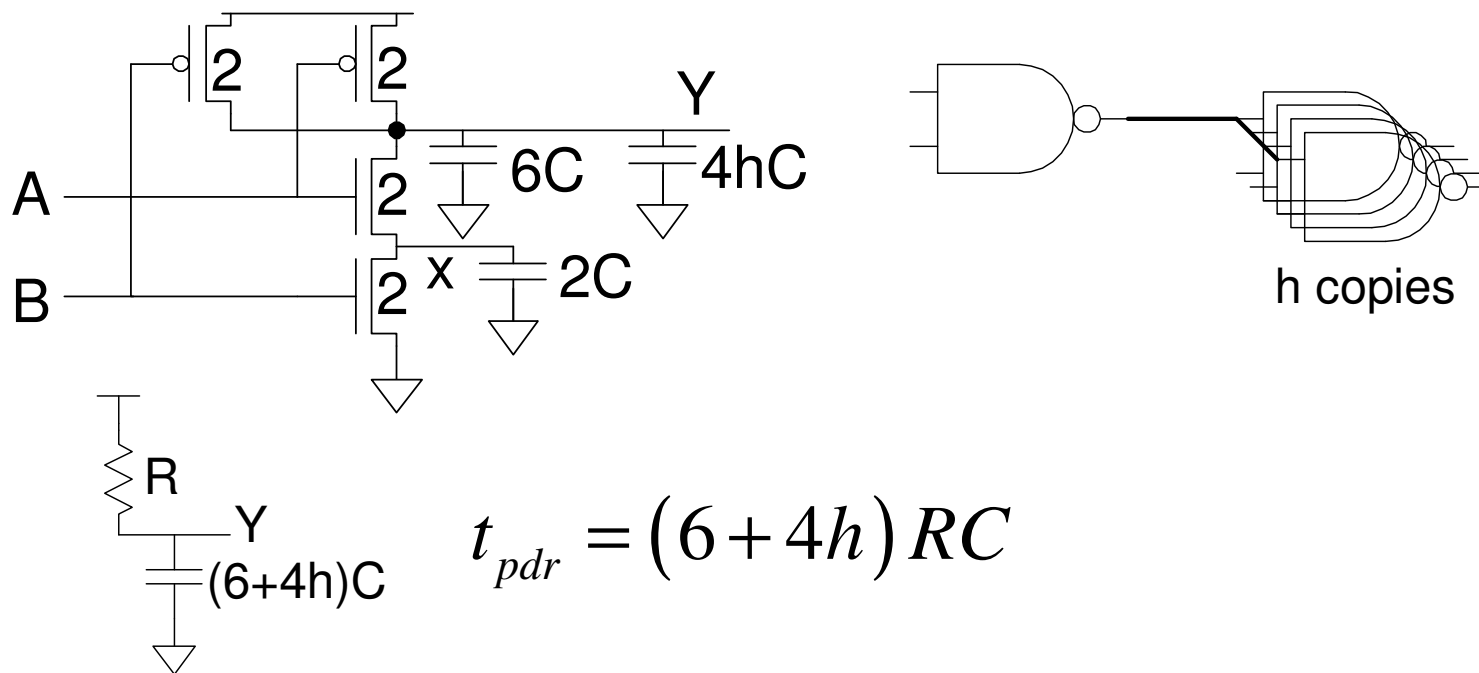
Example: 2-input NAND

- Estimate **rising** and falling propagation delays of a 2-input NAND driving h identical gates.




 
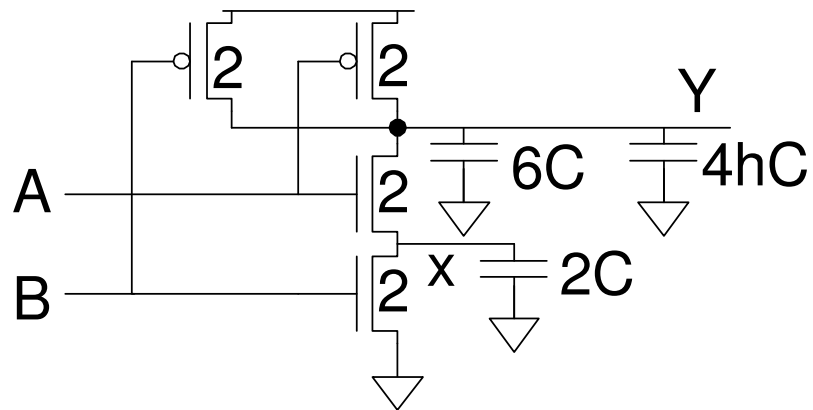
Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



 
 
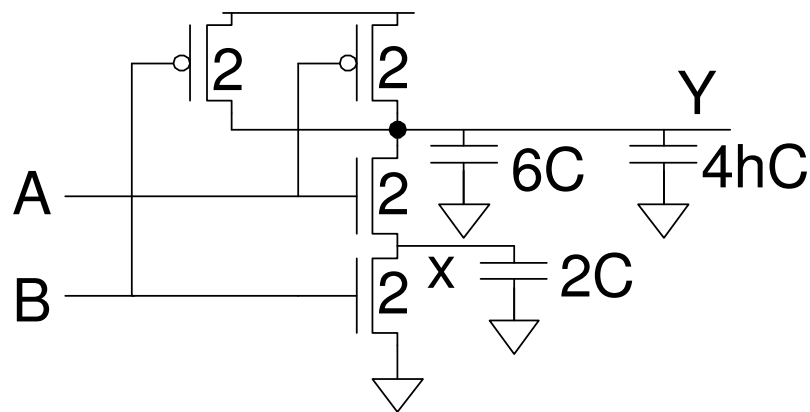
Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.



  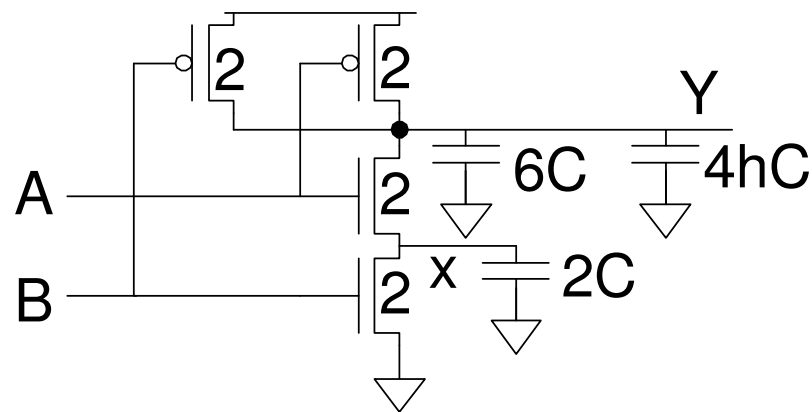Example: 2-input NAND

- Estimate rising and **falling** propagation delays of a 2-input NAND driving h identical gates.





$$\begin{aligned}
 t_{pdf} &= (2C)\left(\frac{R}{2}\right) + \left[(6 + 4h)C\right]\left(\frac{R}{2} + \frac{R}{2}\right) \\
 &= (7 + 4h)RC
 \end{aligned}$$

Delay Components

- Delay has two parts
 - *Parasitic delay*
 - 6 or 7 RC
 - Independent of load
 - *Effort delay*
 - 4h RC
 - Proportional to load capacitance

Contamination Delay

  
- Best-case (contamination) delay can be substantially less than propagation delay.
- Ex: If both inputs fall simultaneously



$$t_{cdr} = (3 + 2h)RC$$



Diffusion Capacitance

 - We assumed contacted diffusion on every s / d.
- Good layout minimizes diffusion area
- Ex: NAND3 layout shares one diffusion contact
 - Reduces output capacitance by $2C$
 - Merged uncontacted diffusion might help too




Layout Comparison

- Which layout is better?

  


Resizing the Inverter

 Minimum-sized
transistor:
 $W=3\lambda$, $L=2\lambda$




To get equal rise and fall times,
 $\beta_n = \beta_p \Rightarrow W_p = 3W_n$, assuming
that electron mobility is three times that
of holes

$$W_p = 9\lambda$$

 

*Sometimes the function
being implemented
makes resizing
unnecessary!*

Analyzing the NAND Gate

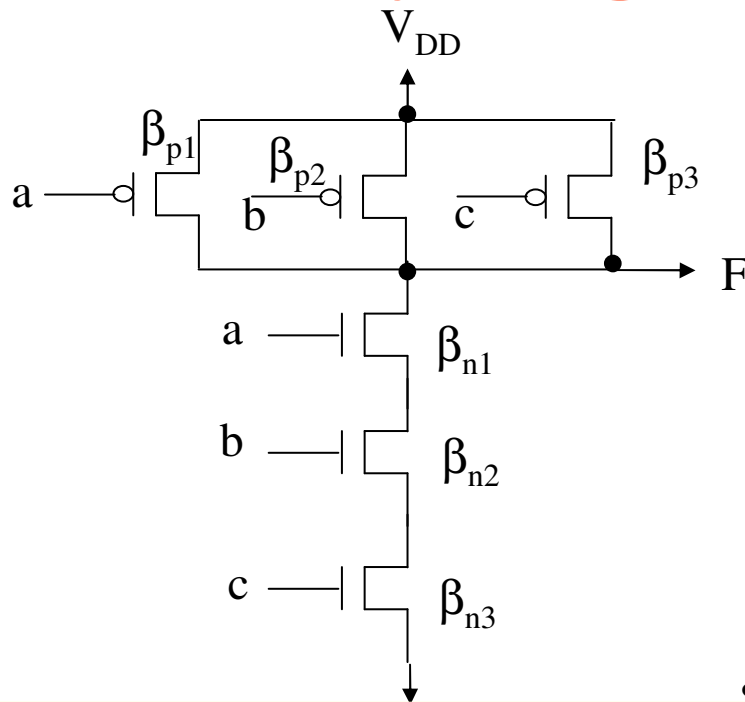

$$\beta_{n, \text{eff}} = \frac{1}{\frac{1}{\beta_{n1}} + \frac{1}{\beta_{n2}} + \frac{1}{\beta_{n3}}}$$

Resistances are in series (conductances are in parallel)

If $\beta_{n1} = \beta_{n2} = \beta_{n3} = \beta_n$ then $\beta_{n, \text{eff}} = \beta_n/3$


- Pull-down circuit has three times resistance, one-third times the conductance

Why not consider resistances in parallel?

For pull-up, only one transistor has to be on, $\beta_{p, \text{eff}} = \min\{\beta_{p1}, \beta_{p2}, \beta_{p3}\}$

If $\beta_{p1} = \beta_{p2} = \beta_{p3} = \beta_p = \beta_n/3$ then $\beta_{n, \text{eff}} = \beta_p \Rightarrow$ no resizing is necessary

Analyzing the NOR Gate

 

$$\beta_{p, \text{eff}} = \frac{1}{\frac{1}{\beta_{p1}} + \frac{1}{\beta_{p2}} + \frac{1}{\beta_{p3}}}$$

Resistances are in series (conductances are in parallel)

If $\beta_{p1} = \beta_{p2} = \beta_{p3} = \beta_p$ then $\beta_{p, \text{eff}} = \beta_p/3$


- Pull-up circuit has three times resistance, one-third times the conductance

For pull-down, only one transistor has to be on, $\beta_{n, \text{eff}} = \min\{\beta_{n1}, \beta_{n2}, \beta_{n3}\}$

If $\beta_{n1} = \beta_{n2} = \beta_{n3} = \beta_n = 3\beta_p$ then $\beta_{n, \text{eff}} = 9\beta_{p, \text{eff}} \Rightarrow$ considerable resizing is necessary


$$W_p = 9W_n!$$

Effect of Series Transistors

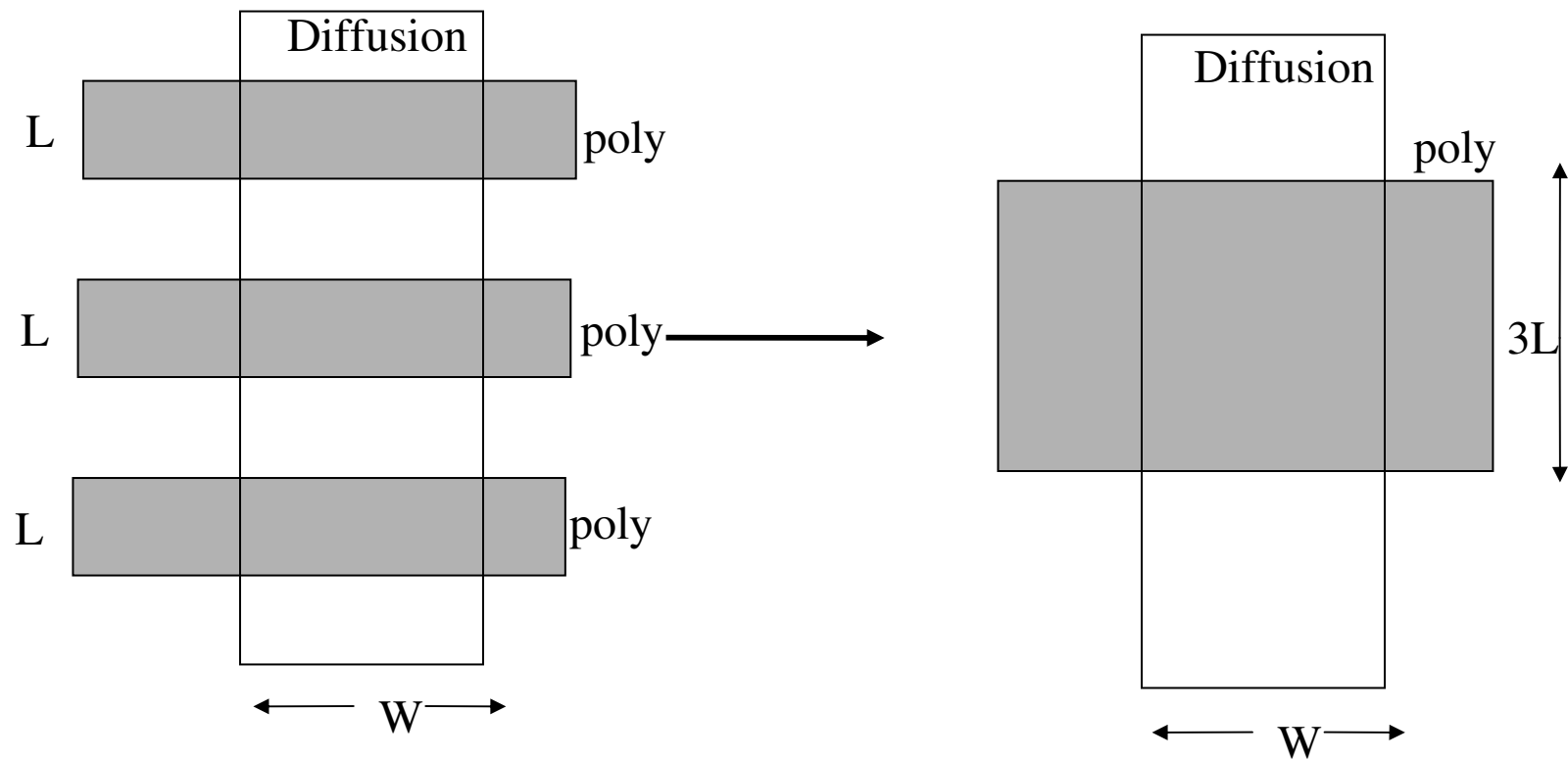

Effect of Series Transistors

Transistor
resizing
example

 

Resize the pull-up transistors to
make pull-up times equal

After resizing:

a: $2\beta_p$, b: $2\beta_p$, c: β_p


Transistor Placement (Series Stack)

How to order transistors in a series stack?

Body effect: $\delta V_t \propto$

$$\sqrt{V_{sb}}$$

 - At time $t = 0$, $a=b=c=0$, $f=1$, capacitances are charged
- Ideally $V_{ta} = V_{tb} = V_{tc} \approx 0.8V$



- However, $V_{ta} > V_{tb} > V_{tc}$ because of body effect


- If a , b , c become 1 at the same time, which transistor will switch on first?

- t_c will switch on first (V_{sb} for t_c is zero), C_c will discharge, pulling V_{sb} for t_b to zero

- If signals arrive at different times, how should the transistors be ordered?

- Design strategy: place latest arriving signal nearest to output-early signals will discharge internal nodes

Transistor Placement

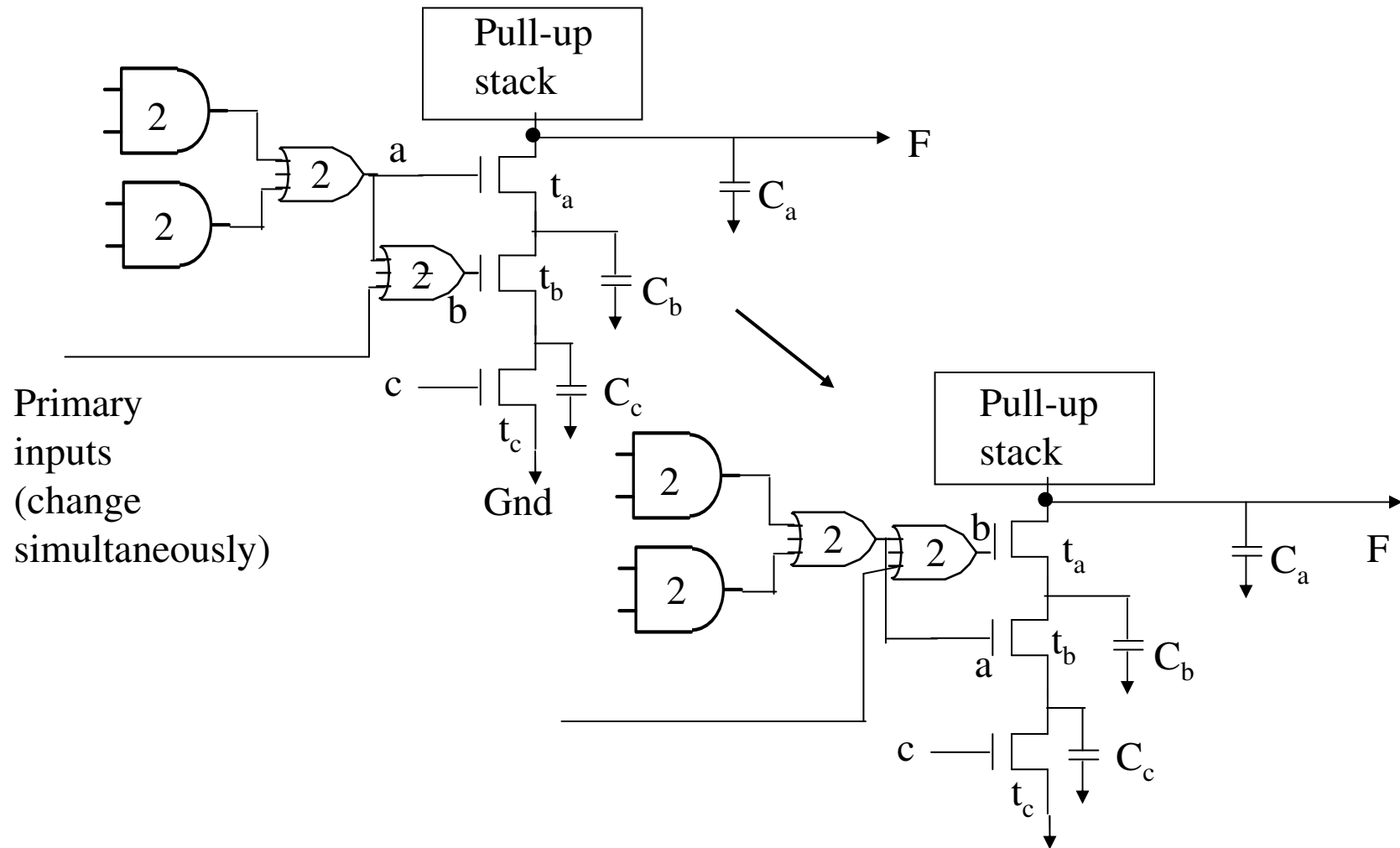


Some Design Guidelines

- Use NAND gates (instead of NOR) wherever possible
- Place inverters (buffers) at high fanout nodes to improve drive capability
- Avoid use of NOR completely in high-speed circuits: $A_1 + A_2 + \dots + A_n = A_1 \cdot A_2 \cdot \dots \cdot A_n$


Some Design Guidelines

 - Use limited fan-in (<10): high fan-in \Rightarrow long series stacks
- Use minimum-sized gates on high fan-out nodes: minimize load presented to driving gate



Logical Effort

- Chip designers face a bewildering array of choices ? ? ?
 - What is the best circuit topology for a function?
 - How many stages of logic give least delay?
 - How wide should the transistors be?
- Logical effort is a method to make these decisions
 - Uses a simple model of delay
 - Allows back-of-the-envelope calculations
 - Helps make rapid comparisons between alternatives
 - Emphasizes remarkable symmetries

 

Example


- Ben Bitdiddle is the memory designer for the Motorola 68W86, an embedded automotive processor. Help Ben design the decoder for a register file.

- Decoder specifications:

- 16 word register file
- Each word is 32 bits wide
- Each bit presents load of 3 unit-sized transistors
- True and complementary address inputs $A[3:0]$
- Each input may drive 10 unit-sized transistors

- Ben needs to decide:

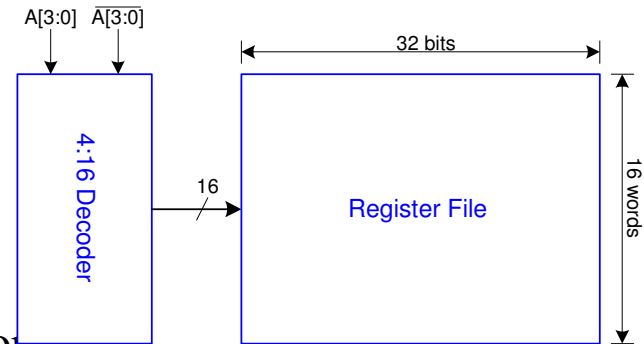- How many stages to use?
- How large should each gate be?
- How fast can decoder operate?



Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

$$\tau = 3RC$$

≈ 12 ps in 180 nm process

40 ps in 0.6 μm process

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- *Effort delay* $f = gh$ (a.k.a. *stage effort*)
 - Again has two components

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. stage effort)
 - Again has two components
- g : *logical effort*
 - Measures relative ability of gate to deliver current
 - $g \equiv 1$ for inverter

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$

- Delay has two components

$$d = f + p$$

- Effort delay $f = gh$ (a.k.a. stage effort)
 - Again has two components
- h : *electrical effort* = C_{out} / C_{in}
 - Ratio of output to input capacitance
 - Sometimes called fanout

Delay in a Logic Gate

- Express delays in process-independent unit

$$d = \frac{d_{abs}}{\tau}$$


- Delay has two components

$$d = f + p$$

- Parasitic delay p
 - Represents delay of gate driving no load
 - Set by internal parasitic capacitance

Delay Plots

$$d = f + p$$
$$= gh + p$$

 


Delay Plots

$$d = f + p$$


$$= gh + p$$

- What about NOR2?

 


Computing Logical Effort

 
- DEF: *Logical effort is the ratio of the input capacitance of a gate to the input capacitance of an inverter delivering the same output current.*
- Measure from delay vs. fanout plots
- Or estimate by counting transistor widths



$$C_{in} = 3$$
$$g = 3/3$$

 

$$C_{in} = 4$$
$$g = 4/3$$

 

$$C_{in} = 5$$
$$g = 5/3$$

Catalog of Gates

- Logical effort of common gates

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		$4/3$	$5/3$	$6/3$	$(n+2)/3$
NOR		$5/3$	$7/3$	$9/3$	$(2n+1)/3$
Tristate / mux	2	2	2	2	2


Catalog of Gates

- Parasitic delay of common gates
 - In multiples of p_{inv} (≈ 1)

Gate type	Number of inputs				
	1	2	3	4	n
Inverter	1				
NAND		2	3	4	n
NOR		2	3	4	n
Tristate / mux	2	4	6	8	2n
XOR, XNOR		4	6	8	

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g =$

Electrical Effort: $h =$


Parasitic Delay: $p =$

Stage Delay: $d =$

Frequency: $f_{\text{osc}} =$

 Example: Ring Oscillator

- Estimate the frequency of an N-stage ring oscillator



Logical Effort: $g = 1$

Electrical Effort: $h = 1$

Parasitic Delay: $p = 1$


Stage Delay: $d = 2$

Frequency: $f_{\text{osc}} = 1/(2*N*d) = 1/4N$

31 stage ring oscillator in
0.6 μm process has
frequency of ~ 200 MHz

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g =$


Electrical Effort: $h =$

Parasitic Delay: $p =$

Stage Delay: $d =$

 Example: FO4 Inverter

- Estimate the delay of a fanout-of-4 (FO4) inverter



Logical Effort: $g = 1$

Electrical Effort: $h = 4$

Parasitic Delay: $p = 1$

Stage Delay: $d = 5$

The FO4 delay is about

200 ps in 0.6 μm process

60 ps in a 180 nm process

$f/3$ ns in an f μm process


Multistage Logic Networks

- Logical effort generalizes to multistage networks

- *Path Logical Effort* $G = \prod g_i$

- *Path Electrical Effort* $H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$

 - *Path Effort* $F = \prod f_i = \prod g_i h_i$




Multistage Logic Networks

- Logical effort generalizes to multistage networks
- *Path Logical Effort* $G = \prod g_i$
- *Path Electrical Effort* $H = \frac{C_{out-path}}{C_{in-path}}$
- *Path Effort* $F = \prod f_i = \prod g_i h_i$
- Can we write $F = GH$?

Paths that Branch

- No! Consider paths that branch:

 

$G =$

$H =$

$GH =$


$h_1 =$

$h_2 =$

$F = GH?$

Paths that Branch

- No! Consider paths that branch:

 

$$G = 1$$

$$H = 90 / 5 = 18$$

$$GH = 18$$

$$h_1 = (15 + 15) / 5 = 6$$

$$h_2 = 90 / 15 = 6$$

$$F = g_1 g_2 h_1 h_2 = 36 = 2GH$$

Branching Effort

- Introduce *branching effort*
 - Accounts for branching between stages in path

$$b = \frac{C_{\text{on path}} + C_{\text{off path}}}{C_{\text{on path}}}$$

$$B = \prod b_i$$

Note:

$$\prod h_i = BH$$

- Now we compute the path effort
 - $F = GBH$

Multistage Delays

- Path Effort Delay $D_F = \sum f_i$
- Path Parasitic Delay $P = \sum p_i$
- Path Delay $D = \sum d_i = D_F + P$

Designing Fast Circuits

$$D = \sum d_i = D_F + P$$

- Delay is smallest when each stage bears same effort

$$\hat{f} = g_i h_i = F^{\frac{1}{N}}$$

- Thus minimum delay of N stage path is

$$D = NF^{\frac{1}{N}} + P$$

- This is a **key** result of logical effort
 - Find fastest possible delay
 - Doesn't require calculating gate sizes

Gate Sizes

- How wide should the gates be for least delay?


$$\hat{f} = gh = g \frac{C_{out}}{C_{in}}$$

$$\Rightarrow C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$


- Working backward, apply capacitance transformation to find input capacitance of each gate given load it drives.
- Check work by verifying input cap spec is met.

 Example: 3-stage path

- Select gate sizes x and y for least delay from A to B



Example: 3-stage path

 

Logical Effort $G =$

Electrical Effort $H =$

Branching Effort $B =$


Path Effort $\hat{F} =$

Best Stage Effort $\hat{f} =$

Parasitic Delay $P =$

Delay $D =$

Example: 3-stage path

 

Logical Effort

$$G = (4/3) * (5/3) * (5/3) = 100/27$$

Electrical Effort

$$H = 45/8$$

Branching Effort

$$B = 3 * 2 = 6$$

Path Effort

$$F = GBH = 125$$

Best Stage Effort

$$\hat{f} = \sqrt[3]{F} = 5$$

Parasitic Delay

$$P = 2 + 3 + 2 = 7$$

Delay


$$D = 3 * 5 + 7 = 22 = 4.4 \text{ FO4}$$

Example: 3-stage path

- Work backward for sizes

$y =$

$x =$

 


Example: 3-stage path

- Work backward for sizes

$$y = 45 * (5/3) / 5 = 15$$


$$x = (15 * 2) * (5/3) / 5 = 10$$

 

Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

D =

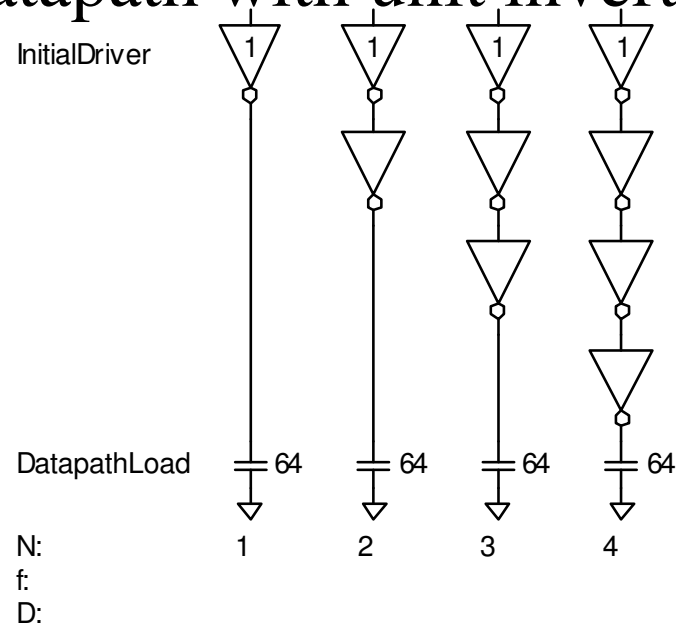


Best Number of Stages

- How many stages should a path use?
 - Minimizing number of stages is not always fastest
- Example: drive 64-bit datapath with unit inverter

$$D = NF^{1/N} + P$$


$$= N(64)^{1/N} + N$$

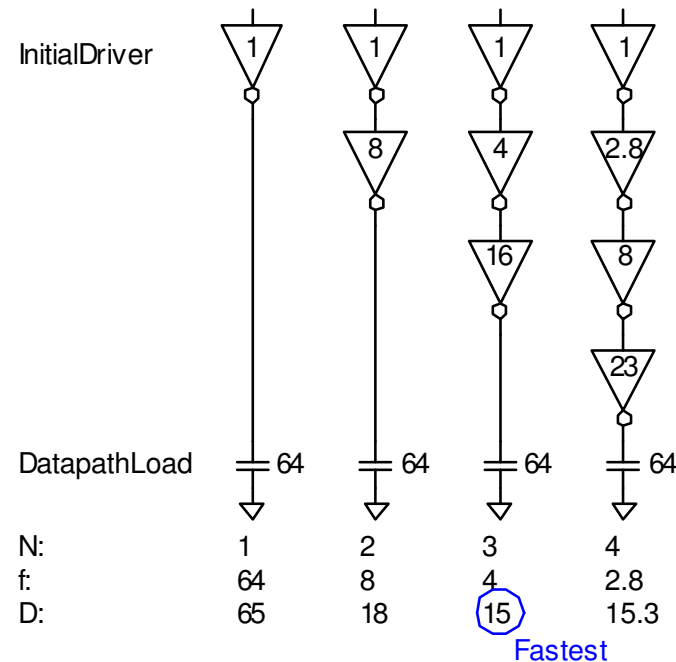

Derivation

- Consider adding inverters to end of path
 - How many give least delay?
 
$$D = NF^{\frac{1}{N}} + \sum_{i=1}^{n_1} p_i + (N - n_1) p_{inv}$$



$$\frac{\partial D}{\partial N} = -F^{\frac{1}{N}} \ln F^{\frac{1}{N}} + F^{\frac{1}{N}} + p_{inv} = 0$$

- Define best stage effort $\rho = F^{\frac{1}{N}}$

$$p_{inv} + \rho(1 - \ln \rho) = 0$$

Best Stage Effort

$$p_{inv} + \rho(1 - \ln \rho) = 0$$

- has no closed-form solution
- Neglecting parasitics ($p_{inv} = 0$), we find $\rho = 2.718$ (e)
- For $p_{inv} = 1$, solve numerically for $\rho = 3.59$

Review of Definitions

Term	Stage	Path
number of stages	1	N
logical effort	g	$G = \prod g_i$
electrical effort	$h = \frac{C_{\text{out}}}{C_{\text{in}}}$	$H = \frac{C_{\text{out-path}}}{C_{\text{in-path}}}$
branching effort	$b = \frac{C_{\text{on-path}} + C_{\text{off-path}}}{C_{\text{on-path}}}$	$B = \prod b_i$
effort	$f = gh$	$F = GBH$
effort delay	f	$D_F = \sum f_i$
parasitic delay	p	$P = \sum p_i$
delay	$d = f + p$	$D = \sum d_i = D_F + P$

Method of Logical Effort

1) Compute path effort

$$F = GBH$$

2) Estimate best number of stages

$$N = \log_4 F$$

3) Sketch path with N stages

4) Estimate least delay

$$D = NF^{\frac{1}{N}} + P$$

5) Determine best stage effort

$$\hat{f} = F^{\frac{1}{N}}$$

6) Find gate sizes

$$C_{in_i} = \frac{g_i C_{out_i}}{\hat{f}}$$

Limits of Logical Effort

- Chicken and egg problem
 - Need path to compute G
 - But don't know number of stages without G
- Simplistic delay model
 - Neglects input rise time effects
- Interconnect
 - Iteration required in designs with wire
- Maximum speed only
 - Not minimum area/power for constrained delay

Summary

- Logical effort is useful for thinking of delay in circuits
 - Numeric logical effort characterizes gates
 - NANDs are faster than NORs in CMOS
 - Paths are fastest when effort delays are ~ 4
 - Path delay is weakly sensitive to stages, sizes
 - But using fewer stages doesn't mean faster paths
 - Delay of path is about $\log_4 F$ FO4 inverter delays
 - Inverters and NAND2 best for driving large caps
- Provides language for discussing fast circuits
 - But requires practice to master

Power and Energy

- Power is drawn from a voltage source attached to the V_{DD} pin(s) of a chip.

$$P(t) = i_{DD}(t)V_{DD}$$

- Instantaneous Power:

$$E = \int_0^T P(t)dt = \int_0^T i_{DD}(t)V_{DD}dt$$


- Energy:

$$P_{\text{avg}} = \frac{E}{T} = \frac{1}{T} \int_0^T i_{DD}(t)V_{DD}dt$$

- Average Power:


Dynamic Power

 - Dynamic power is required to charge and discharge load capacitances when transistors switch.
- One cycle involves a rising and falling output.
- On rising output, charge $Q = CV_{DD}$ is required
- On falling output, charge is dumped to GND
- This repeats $T_{f_{sw}}$ times over an interval of T



Dynamic Power Cont.

$$P_{\text{dynamic}} =$$

 


Dynamic Power Cont.

$$P_{\text{dynamic}} = \frac{1}{T} \int_0^T i_{DD}(t) V_{DD} dt$$

$$= \frac{V_{DD}}{T} \int_0^T i_{DD}(t) dt$$

$$= \frac{V_{DD}}{T} [T f_{\text{sw}} C V_{DD}]$$

$$= C V_{DD}^2 f_{\text{sw}}$$

 

Activity Factor

- Suppose the system clock frequency = f
- Let $f_{sw} = \alpha f$, where α = activity factor
 - If the signal is a clock, $\alpha = 1$
 - If the signal switches once per cycle, $\alpha = 1/2$
 - Dynamic gates:
 - Switch either 0 or 2 times per cycle, $\alpha = 1/2$
 - Static gates:
 - Depends on design, but typically $\alpha = 0.1$

- Dynamic power: $P_{dynamic} = \alpha C V_{DD}^2 f$

Short Circuit Current

- When transistors switch, both nMOS and pMOS networks may be momentarily ON at once
- Leads to a blip of “short circuit” current.
- $< 10\%$ of dynamic power if rise/fall times are comparable for input and output

Example

- 200 Mtransistor chip
 - 20M logic transistors
 - Average width: 12λ
 - 180M memory transistors
 - Average width: 4λ
 - 1.2 V 100 nm process
 - $C_g = 2 \text{ fF}/\mu\text{m}$

Dynamic Example

- Static CMOS logic gates: activity factor = 0.1
- Memory arrays: activity factor = 0.05 (many banks!)
- Estimate dynamic power consumption per MHz. Neglect wire capacitance and short-circuit current.

Dynamic Example

- Static CMOS logic gates: activity factor = 0.1
- Memory arrays: activity factor = 0.05 (many banks!)
- Estimate dynamic power consumption per MHz. Neglect wire capacitance.

$$C_{\text{logic}} = (20 \times 10^6)(12\lambda)(0.05\mu\text{m} / \lambda)(2\text{fF} / \mu\text{m}) = 24\text{nF}$$

$$C_{\text{mem}} = (180 \times 10^6)(4\lambda)(0.05\mu\text{m} / \lambda)(2\text{fF} / \mu\text{m}) = 72\text{nF}$$

$$P_{\text{dynamic}} = [0.1C_{\text{logic}} + 0.05C_{\text{mem}}](1.2)^2 f = 8.6\text{ mW/MHz}$$

Static Power

- Static power is consumed even when chip is quiescent.
 - Ratioed circuits burn power in fight between ON transistors
 - Leakage draws power from nominally OFF devices

$$I_{ds} = I_{ds0} e^{\frac{V_{gs} - V_t}{nV_T}} \left[1 - e^{\frac{-V_{ds}}{V_T}} \right]$$

$$V_t = V_{t0} - \eta V_{ds} + \gamma \left(\sqrt{\phi_s + V_{sb}} - \sqrt{\phi_s} \right)$$

Ratio Example

- The chip contains a 32 word x 48 bit ROM
 - Uses pseudo-nMOS decoder and bitline pullups
 - On average, one wordline and 24 bitlines are high
- Find static power drawn by the ROM
 - $\beta = 75 \mu\text{A}/\text{V}^2$
 - $V_{tp} = -0.4\text{V}$

Ratio Example

- The chip contains a 32 word x 48 bit ROM
 - Uses pseudo-nMOS decoder and bitline pullups
 - On average, one wordline and 24 bitlines are high
- Find static power drawn by the ROM
 - $\beta = 75 \mu\text{A}/\text{V}^2$
 - $V_{tp} = -0.4\text{V}$

- Solution:
$$I_{\text{pull-up}} = \beta \frac{(V_{DD} - |V_{tp}|)^2}{2} = 24\mu\text{A}$$
$$P_{\text{pull-up}} = V_{DD} I_{\text{pull-up}} = 29\mu\text{W}$$
$$P_{\text{static}} = (31 + 24)P_{\text{pull-up}} = 1.6 \text{ mW}$$

Leakage Example

- The process has two threshold voltages and two oxide thicknesses.
- Subthreshold leakage:
 - 20 nA/ μm for low V_t
 - 0.02 nA/ μm for high V_t
- Gate leakage:
 - 3 nA/ μm for thin oxide
 - 0.002 nA/ μm for thick oxide
- Memories use low-leakage transistors everywhere
- Gates use low-leakage transistors on 80% of logic

Leakage Example Cont.

- Estimate static power:

Leakage Example Cont.

- Estimate static power:

- High leakage: $(20 \times 10^6)(0.2)(12\lambda)(0.05 \mu m / \lambda) = 2.4 \times 10^6 \mu m$

- Low leakage: $(20 \times 10^6)(0.8)(12\lambda)(0.05 \mu m / \lambda) +$
 $(180 \times 10^6)(4\lambda)(0.05 \mu m / \lambda) = 45.6 \times 10^6 \mu m$

$$I_{static} = (2.4 \times 10^6 \mu m) \left[(20 nA / \mu m) / 2 + (3 nA / \mu m) \right] +$$
$$(45.6 \times 10^6 \mu m) \left[(0.02 nA / \mu m) / 2 + (0.002 nA / \mu m) \right]$$
$$= 32 mA$$

$$P_{static} = I_{static} V_{DD} = 38 mW$$

Leakage Example Cont.

- Estimate static power: $(20 \times 10^6)(0.2)(12\lambda)(0.05 \mu m / \lambda) = 2.4 \times 10^6 \mu m$
 - High leakage: $(20 \times 10^6)(0.8)(12\lambda)(0.05 \mu m / \lambda) +$
 - Low leakage: $(180 \times 10^6)(4\lambda)(0.05 \mu m / \lambda) = 45.6 \times 10^6 \mu m$

$$I_{static} = (2.4 \times 10^6 \mu m) \left[(20 nA / \mu m) / 2 + (3 nA / \mu m) \right] + \\ (45.6 \times 10^6 \mu m) \left[(0.02 nA / \mu m) / 2 + (0.002 nA / \mu m) \right] \\ = 32 mA$$

$$P_{static} = I_{static} V_{DD} = 38 mW$$

- If no low leakage devices, $P_{static} = 749 mW (!)$

Low Power Design

- Reduce dynamic power
 - α :
 - C:
 - V_{DD} :
 - f:
- Reduce static power

Low Power Design

- Reduce dynamic power
 - α : clock gating, sleep mode
 - C:
 - V_{DD} :
 - f:
- Reduce static power

Low Power Design

- Reduce dynamic power
 - α : clock gating, sleep mode
 - C : small transistors (esp. on clock), short wires
 - V_{DD} :
 - f :
- Reduce static power

Low Power Design

- Reduce dynamic power
 - α : clock gating, sleep mode
 - C : small transistors (esp. on clock), short wires
 - V_{DD} : lowest suitable voltage
 - f :
- Reduce static power

Low Power Design

- Reduce dynamic power
 - α : clock gating, sleep mode
 - C: small transistors (esp. on clock), short wires
 - V_{DD} : lowest suitable voltage
 - f: lowest suitable frequency
- Reduce static power

Low Power Design

- Reduce dynamic power
 - α : clock gating, sleep mode
 - C: small transistors (esp. on clock), short wires
 - V_{DD} : lowest suitable voltage
 - f: lowest suitable frequency
- Reduce static power
 - Selectively use ratioed circuits
 - Selectively use low V_t devices
 - Leakage reduction:
stacked devices, body bias, low temperature