

CMOS Testing: Part 1

- Introduction
- Fault models
 - Stuck-line (single and multiple)
 - Bridging
 - Stuck-open
- Test pattern generation
 - Combinational circuit test generation
 - Sequential circuit test generation

Outline

- Testing
 - Logic Verification
 - Silicon Debug
 - Manufacturing Test
- Fault Models
- Observability and Controllability
- Design for Test
 - Scan
 - BIST
- Boundary Scan

Testing

- Testing is one of the most expensive parts of chips
 - Logic verification accounts for $> 50\%$ of design effort for many chips
 - Debug time after fabrication has enormous cost
 - Shipping defective parts can sink a company
- Example: Intel FDIIV bug
 - Logic error not caught until $> 1\text{M}$ units shipped
 - Recall cost \$450M (!!!)

Logic Verification

- Does the chip simulate correctly?
 - Usually done at HDL level
 - Verification engineers write test bench for HDL
 - Can't test all cases
 - Look for corner cases
 - Try to break logic design
- Ex: 32-bit adder
 - Test all combinations of corner cases as inputs:
 - 0, 1, 2, $2^{31}-1$, -1, -2^{31} , a few random numbers
- Good tests require ingenuity

Silicon Debug

- Test the first chips back from fabrication
 - If you are lucky, they work the first time
 - If not...
- Logic bugs vs. electrical failures
 - Most chip failures are logic bugs from inadequate simulation
 - Some are electrical failures
 - Crosstalk
 - Dynamic nodes: leakage, charge sharing
 - Ratio failures
 - A few are tool or methodology failures (e.g. DRC)
- Fix the bugs and fabricate a corrected chip

Shmoo Plots

*Clock period in ns on the left, frequency increases going up
Voltage on the bottom, increase left to right*

** indicates a failure*




- How to diagnose failures?

- Hard to access chips

- Picoprobes
- Electron beam
- Laser voltage probing
- Built-in self-test

- Shmoo plots

   - Vary voltage, frequency
- Look for cause of electrical failures



Need for Testing

- Physical defects are likely in manufacturing
 - Missing connections (opens)
 - Bridged connections (shorts)
 - Imperfect doping, processing steps
 - Packaging
- Yields are generally low
 - Yield = Fraction of good die per wafer
- Need to weed out bad die before assembly
- Need to test during operation
 - Electromagnetic interference, mechanical stress, electromigration, alpha particles


Manufacturing Test

- A speck of dust on a wafer is sufficient to kill chip
- *Yield* of any chip is $< 100\%$
 - Must test chips after manufacturing before delivery to customers to only ship good p
- Manufacturing testers are very expensive
 - Minimize time on tester
 - Careful selection of *test vectors*



Testing Your Chips

 - If you don't have a multimillion dollar tester:
 - Build a breadboard with LED's and switches
 - Hook up a logic analyzer and pattern generator
 - Or use a low-cost functional chip tester



Testing Levels and Test Costs

- Wafer
 - Packaged chip
 - Board
 - System
 - Field
 - Concurrent checking
- Cost to detect a fault (per chip)
 - Wafer: \$0.01-\$0.1
 - Packaged chip: \$0.1-\$1
 - Board: \$1-\$10
 - System: \$10-\$100
 - Field: \$100-1000

Manufacturing Testing

Goal: Detect manufacturing defects

Defects: layer-to-layer shorts
discontinuous wires
thin-oxide shorts to substrate or well



Faults: nodes shorted to power or ground (stuck-at)
nodes shorted to each other (bridging)
inputs floating, outputs disconnected (stuck-open)

Fault
models


Testing : The Buzzwords

- Errors
 - Permanent
 - Intermittent
 - Transient
- Faults
 - Physical
 - Logical
- Test Evaluation
 - Fault coverage
 - Fault simulation
- Types of testing
 - Off-line, on-line
 - Self-test vs external test
 - DC (static) vs AC (at-speed)
 - Edge-pin, guided-probe, bed-of-nails, E-beam, in-circuit

Testing and Diagnosis

- Testing: Determine if the system (chip, board) is behaving correctly
- Diagnosis: Locate the cause of malfunctioning

Testing and Diagnosis

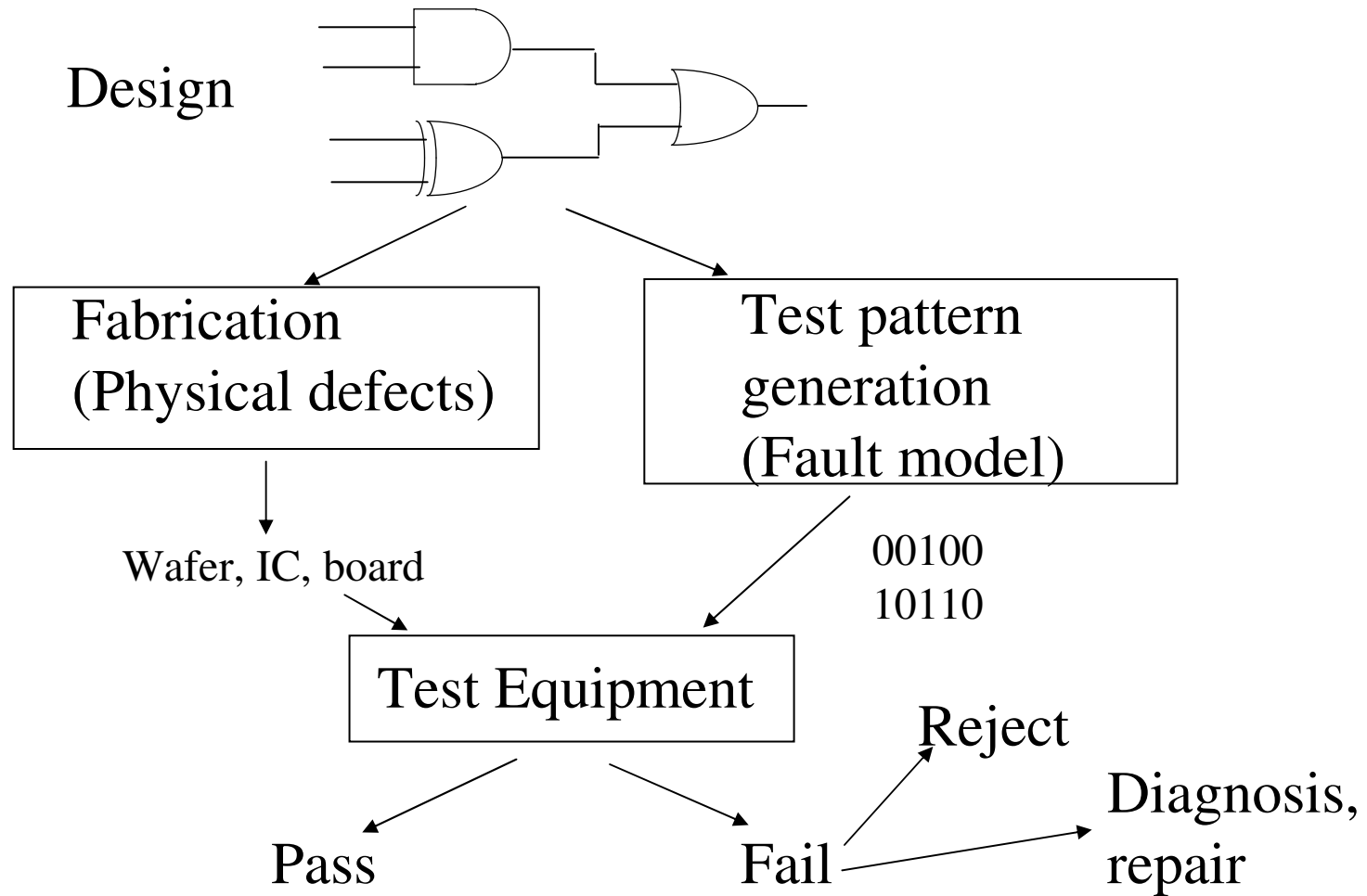

Testing: The Inevitable

Acronyms



- System under test
 - UUT: Unit Under Test
 - CUT: Circuit Under Test
 - DUT: Device Under Test
- The tester
 - ATE: Automatic Test Equipment
- Test generation
 - ATPG: Automatic Test Pattern Generation
- Fault Models
 - SSL: Single Stuck-Line
 - MSL: Multiple Stuck-Line
 - BF: Bridging Fault
- DFT: Design for Testability
 - BIST: Built-in self-test
 - LFSR: Linear-Feedback Shift-Register

Fault Models

- Defects are too many and too difficult to explicitly enumerate
- Abstraction (technology independence): presence of physical defect is modeled by changing the logic function (or delay)
- Reduced complexity: distinct physical defects may be represented by the same logical fault
- Generality: tests derived for logical faults may detect vaguely-understood or hard-to-analyze physical defects
- A *test pattern* detects a fault from the fault model

Single Stuck-Line (SSL) Model

  - A single node in the circuit is stuck-at 1 (s-a-1) or 0 (s-a-0).



Fault-free function $z = AB + CD$

Faulty function $z^f = AB$

Fault-free function $z = AB + CD$

Faulty function $z^f = AB + D$




Number of possible stuck-at faults in a circuit with n lines?

Number of faults reduced by finding equivalent classes

Stuck-At Faults



- How does a chip fail?
 - Usually failures are shorts between two conductors or opens in a conductor
 - This can cause very complicated behavior
- A simpler model: *Stuck-At*
 - Assume all failures cause nodes to be “stuck-at” 0 or 1, i.e. shorted to GND or V_{DD}
 - Not quite true, but works well in practice

Examples

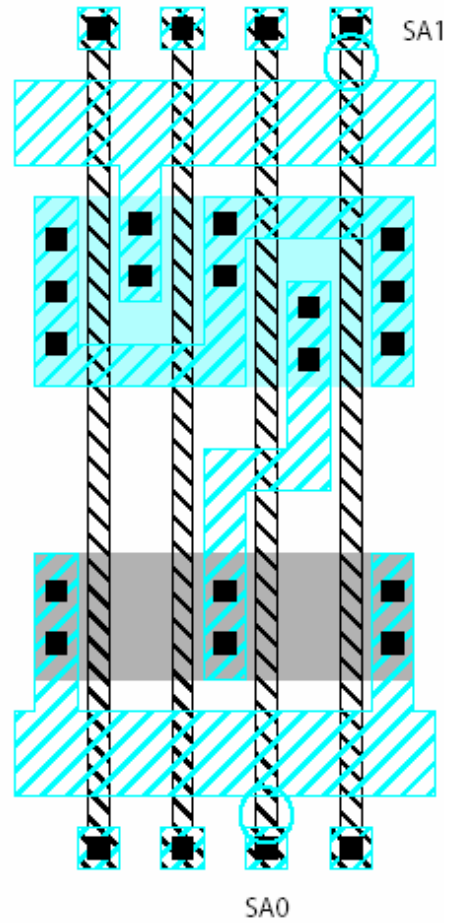  

SSL Fault Detection

  
- A test pattern for fault x s-a- d is an input combination that 1) places \bar{d} on x (activation), 2) propagates fault effect (D or \bar{D}) to primary output



$ABCE = 0011$ is a test pattern for C s-a-0

Multiple Stuck-Line (MSF) Faults

 - More than one line may be stuck at a logic value



Fault: {C s-a-0, x s-a-1}

How many MSL fault can there be in a circuit with n nodes?

How to get test patterns for MSL faults?

Fault universe is too large, MSL fault model seldom used, especially since tests for SSL faults cover many MSL faults

Observability & Controllability

- *Observability*: ease of observing a node by watching external output pins of the chip
- *Controllability*: ease of forcing a node to 0 or 1 by driving input pins of the chip
- Combinational logic is usually easy to observe and control
- Finite state machines can be very difficult, requiring many cycles to enter desired state
 - Especially if state transition diagram is not known to the test engineer


Test Pattern Generation

- Manufacturing test ideally would check every node in the circuit to prove it is not stuck.
- Apply the smallest sequence of test vectors necessary to prove each node is not stuck.
- Good observability and controllability reduces number of test vectors required for manufacturing test.
 - Reduces the cost of testing
 - Motivates design-for-test

Test Pattern Generation

- Exhaustive testing: Apply 2^n pattern to n -input circuit
- Not practical for large n
- Advantage: Fault-model independent

 Fault-Oriented Test Generation Algorithm:



- 1) Set x to 1: activate fault
- 2) Justify D on x, propagate D

to z

Set C and D to 1

Set y to 0


Set either A or B to 0

Example test pattern: ABCD = 0011

- Backtracking may be necessary
- Test generation is NP-complete

Test Example


	SA1	SA0
• A_3	{0110}	{1110}
• A_2	{1010}	{1110}
• A_1	{0100}	{0110}
• A_0	{0110}	{0111}
• n1	{1110}	{0110}
• n2	{0110}	{0100}
• n3	{0101}	{0110}
• Y	{0110}	{1110}

 

- Minimum set: {0100, 0101, 0110, 0111, 1010, 1110}

Bridging Faults

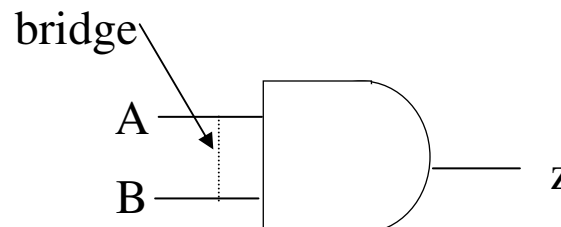- Models short circuits, pairs of nodes considered
- Number of bridging faults?
- Feedback vs non-feedback bridging faults




A	B	z	z^f	Wired-AND	Wired-OR
0	0	0	0	0	0
0	1	0	?	0	1
1	0	1	?	0	1
1	1	1	1	1	1

$z^f = ?$

What are the test patterns in this example?

Stuck-Open Faults

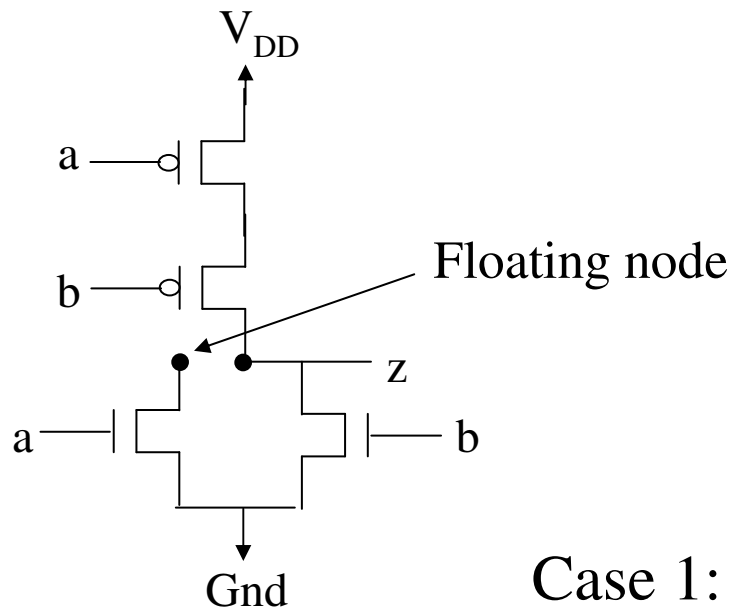

Fault-free circuit: $z = \overline{a+b}$

Faulty circuit: $z^f = \overline{a+b} + \overline{ab}\tilde{z}$


\tilde{z} : Previous value of z

Case 1: $a = b = 1$, z pulled down to 0

Case 2: $a = 1$, $b = 0$, z retains previous state

A test for a stuck-open fault requires two patterns
{ $ab = 00$, $ab = 10$ }

Sequential Circuit Test Generation

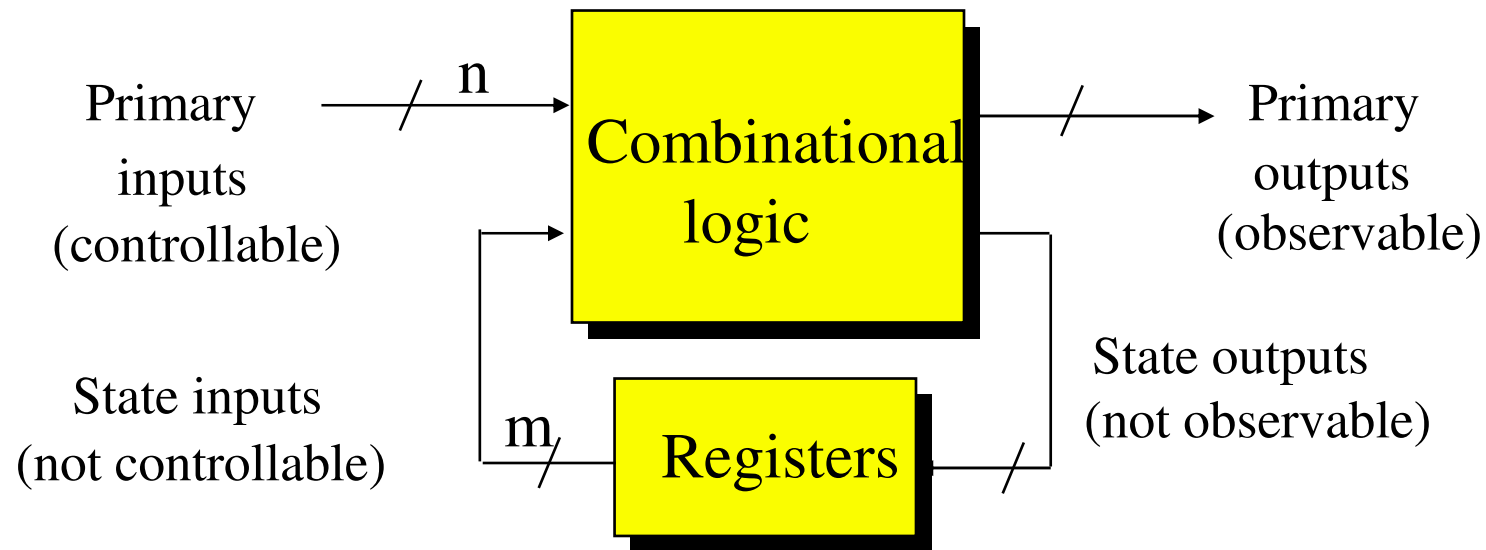

- Difficult problem!
- Exhaustive testing requires 2^{m+n} patterns (2^m states and 2^n transitions from each state)
- Every fault requires a sequence of patterns


Initializing sequence: drive to known state

Test activation



Propagation sequence: propagate discrepancy to observable output

Sequential Circuit Test Generation

 
- Iterative-array model (pseudo-combinational circuit)



Sequential Circuit Test Generation

 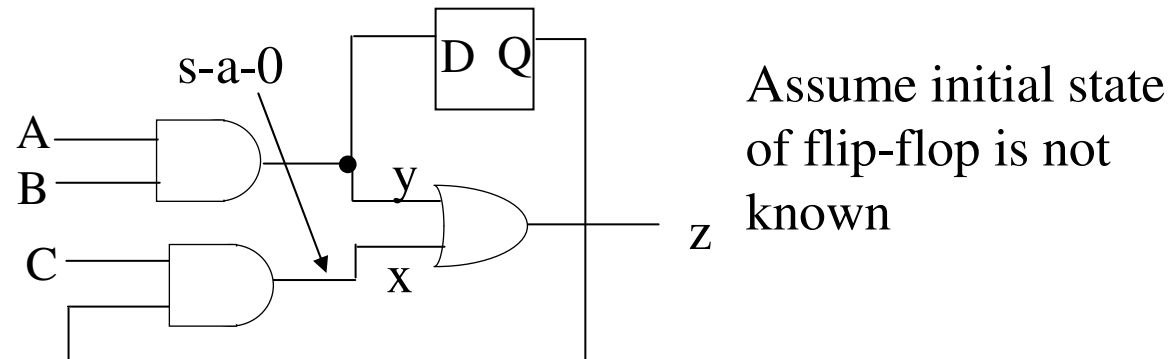

ABC = 11X

 

ABC = 011

Current time frame

Backward
traversal
in time

Test pattern sequence: {11X, 011}

Summary

- Think about testing from the beginning
 - Simulate as you go
 - Plan for test after fabrication
- “If you don’t test it, it won’t work! (Guaranteed)”