

ECE 538

VLSI System Testing

Krish Chakrabarty


Logic Simulation

Introduction

- Motivation
- Types of logic simulation
 - Compiled code
 - Event-driven
- Delay models
- Element evaluation
- Hazard detection

Motivation

 - A design verification technique (functional and timing)
- Compare results obtained with expected responses specified by the specification
- Use software model



Motivation

- Correctness, independent of initial (power-on) state
- Insensitive to small variations in component delays
- Free of races, oscillations, “illegal” input combinations, “unsafe” states
- Evaluation of design alternatives (what-if scenarios)
- Documentation (generation of timing diagrams)


Logic Simulation

- What is simulation?
- Design verification
- Circuit modeling
- True-value simulation algorithms
 - Compiled-code simulation
 - Event-driven simulation
- Summary

Simulation Defined

- Definition: Simulation refers to modeling of a design, its function and performance.
- A software simulator is a computer program; an emulator is a hardware simulator.
- Simulation is used for design verification:
 - Validate assumptions
 - Verify logic
 - Verify performance (timing)
- Types of simulation:
 - Logic or switch level
 - Timing
 - Circuit
 - Fault

Simulation for Verification

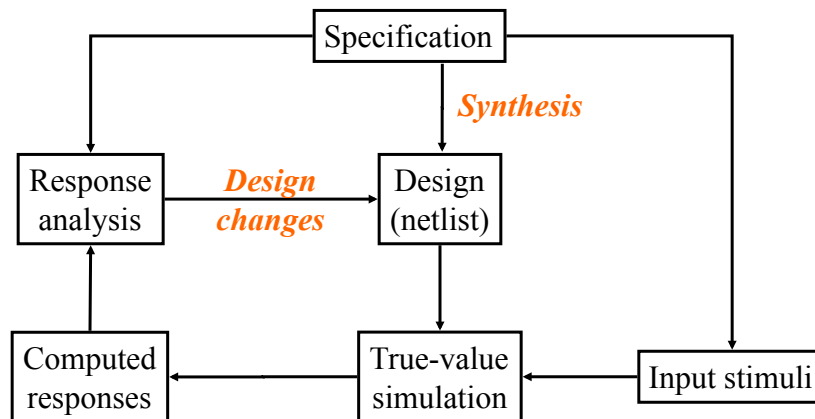

ECE 538

Krish Chakrabarty

7

Modeling for Simulation


- **Modules, blocks or components described by**
 - Input/output (I/O) function
 - Delays associated with I/O signals
 - Examples: binary adder, Boolean gates, FET, resistors and capacitors
- **Interconnects represent**
 - ideal signal carriers, or
 - ideal electrical conductors
- **Netlist: a format (or language) that describes a design as an interconnection of modules. Netlist may use hierarchy.**

ECE 538


Krish Chakrabarty

8

Example: A Full-Adder


 


 HA;
inputs: a, b;
outputs: c, f;
AND: A1, (a, b), (c);
AND: A2, (d, e), (f);
OR: O1, (a, b), (d);
NOT: N1, (c), (e);



FA;
inputs: A, B, C;
outputs: Carry, Sum;
HA: HA1, (A, B), (D, E);
HA: HA2, (E, C), (F, Sum);
OR: O2, (D, F), (Carry);

Logic Model of MOS Circuit

 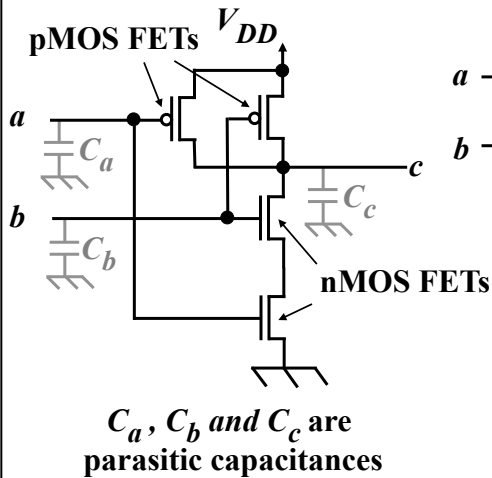


D_a and D_b are interconnect or propagation delays

D_c is inertial delay of gate


Options for Inertial Delay

(simulation of a NAND gate)

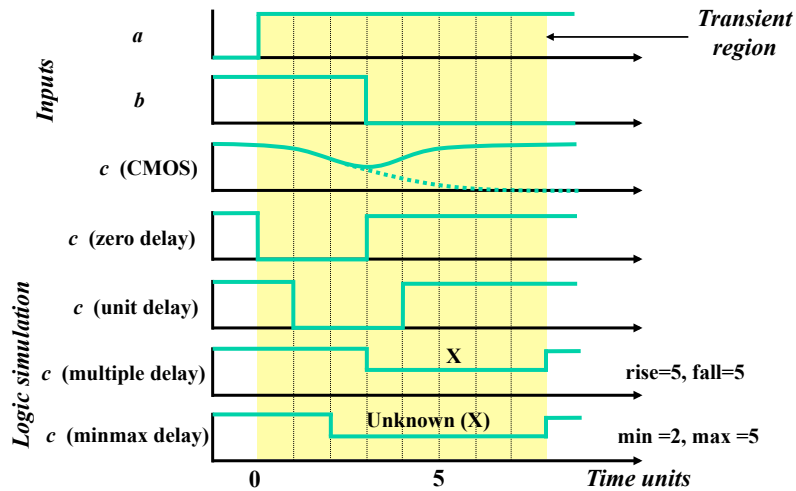

Signal States

 - Two-states (0, 1) can be used for purely combinational logic with zero-delay.
- Three-states (0, 1, X) are essential for timing hazards and for sequential logic initialization.
- Four-states (0, 1, X, Z) are essential for MOS devices. See example below.
- Analog signals are used for exact timing of digital logic and for analog circuits.



Modeling Levels

Modeling level	Circuit description	Signal values	Timing	Application
Function, behavior, RTL	Programming language-like HDL	0, 1	Clock boundary	Architectural and functional verification
Logic	Connectivity of Boolean gates, flip-flops and transistors	0, 1, X and Z	Zero-delay unit-delay, multiple-delay	Logic verification and test
Switch	Transistor size and connectivity, node capacitances	0, 1 and X	Zero-delay	Logic verification
Timing	Transistor technology data, connectivity, node capacitances	Analog voltage	Fine-grain timing	Timing verification
Circuit	Tech. Data, active/passive component connectivity	Analog voltage, current	Continuous time	Digital timing and analog circuit verification

ECE 538

Krish Chakrabarty

13

True-Value Simulation Algorithms

- Compiled-code simulation (oblivious simulation)
 - Applicable to zero-delay combinational logic
 - Also used for cycle-accurate synchronous sequential circuits for logic verification
 - Efficient for highly active circuits, but inefficient for low-activity circuits
 - High-level (e.g., C language) models can be used
- Event-driven simulation (exclusive simulation of activity)
 - Only gates or modules with input events are evaluated (*event means a signal change*)
 - Delays can be accurately simulated for timing verification
 - Efficient for low-activity circuits
 - Can be extended for fault simulation

ECE 538

Krish Chakrabarty

14

Types of Simulation (Contd.)

- Compiled-code (oblivious)
 - The circuit is described in a programming language and an executable model is generated
 - Circuit operation \equiv program execution
 - Fast and efficient but inflexible; practical only for small circuits
- Event-driven
 - Exclusive simulation of activity
 - Circuit is a data structure, simulation program is same for all circuits
 - Flexible, but requires event list management (overhead)


Compiled-Code Algorithm

- Step 1: Levelize combinational logic and encode in a compilable programming language
- Step 2: Initialize internal state variables (flip-flops)
- Step 3: For each input vector
 - Set primary input variables
 - Repeat (until steady-state or max. iterations)
 - Execute compiled code
 - Report or save computed variables

Compiled-Code Simulation


```
LDA B
AND Q
INV
STA E
OR A
STA F
STA Q
```

Simulation program

 


- Delays can be modeled by explicitly adding them to the software model

Event-Driven Simulation

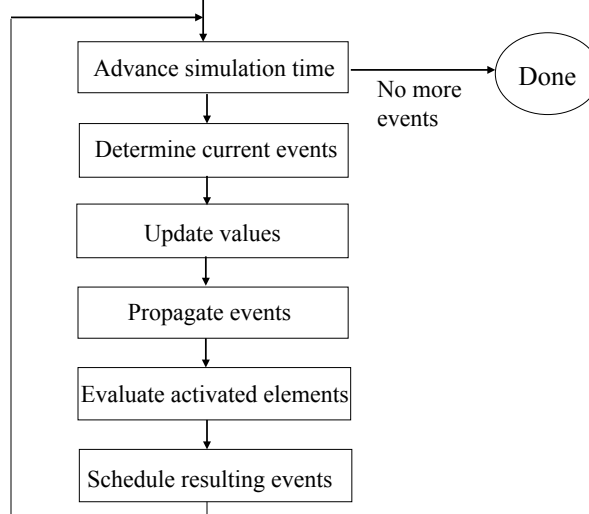


Event-Driven Simulation

 

Snapshot of event list

t = 0		t = 2		t = 4	
Event	Time	Event	Time	Event	Time
F = 1	t = 2	G = 1	t = 4	Y = 1	t = 7
		Z = 1	t = 4		


Event-Driven Algorithm (Example)

 

Time stack

	Scheduled events	Activity list
t = 0	c = 0	d, e
1		
2	d = 1, e = 0	f, g
3		
4	g = 0	
5		
6	f = 1	g
7		
8	g = 1	

Time Wheel (Circular Stack)

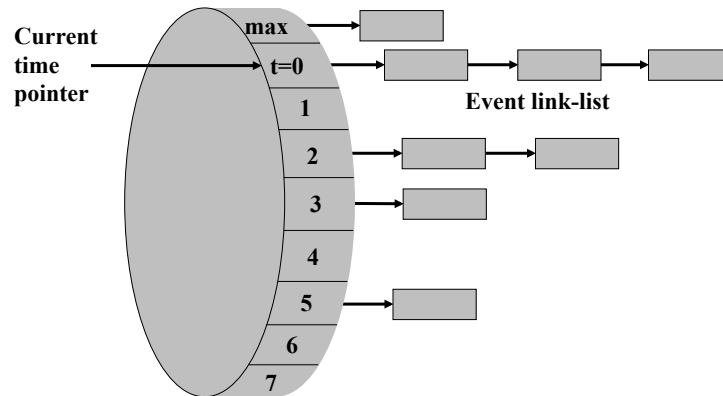


ECE 538

Krish Chakrabarty

21

Efficiency of Event-driven Simulator

- Simulates events (value changes) only
- Speed up over compiled-code can be ten times or more; in large logic circuits about 0.1 to 10% gates become active for an input change

 

ECE 538

Krish Chakrabarty


22

Delay Models

- Transport delay (pure delay)
 - Single delay value for each gate
- Rise/fall times
 - Two delay values for each gate output
- Ambiguity delay
 - Min and max delay values for each gate
 - Ambiguity region becomes enlarged towards primary outputs
- Inertial delay
 - Filter out narrow pulses (spikes and glitches)

Element Evaluation

 - Simulation speed depends on fast elements (gates) that can be evaluated
- Truth tables
 - $O(1)$ evaluation but $O(2^N)$ storage
 - Decision step needed (which truth table?)
- Zoom table of size tS combines t individual truth tables, S is size of largest truth table



Input Scanning

evaluate (G,c,i)

begin

u_values = FALSE;

for every input value of G

begin

if $v = c$ then return $c \oplus i$

if $v = u$ then *u_values* = TRUE

end

if *u_values* return u

return $\bar{c} \oplus i$

end

O(1) storage, O(N) evaluation

• Controlling value c

• Inversion value i

c	X	X	c ⊕ i
X	c	X	c ⊕ i
X	X	c	c ⊕ i
\bar{c}	\bar{c}	\bar{c}	$\bar{c} \oplus i$

	c	i
AND	0	0
OR	1	0
NAND	0	1
NOR	1	1

Input Counting

- Maintain two counters *c_count* and *u_count* for every gate
 - *c_count*: number of inputs with c values
 - *u_count*: number of inputs with u values
- These counters must be updated

evaluate (G,c,i)

begin

if *c_count* > 0 then return $c \oplus i$

if *u_count* > 0 then return u


return $\bar{c} \oplus i$

end


• O(1) storage

• O(1) evaluation

Hazard Detection

 

 - Simulator should detect hazards (analyze transient behavior of signals)
- 3-valued logic simulation:



- How many logic values are necessary?
- More the better, but...more complexity

Summary

- Logic or true-value simulators are essential tools for design verification.
- Verification vectors and expected responses are generated (often manually) from specifications.
- A logic simulator can be implemented using either compiled-code or event-driven method.
- Per vector complexity of a logic simulator is approximately linear in circuit size.
- Modeling level determines the evaluation procedures used in the simulator.