

ECE 538

VLSI System Testing

Krish Chakrabarty

Test Generation: Part 1

Introduction

- Classification of test generation methods
- Fault table analysis
- Boolean difference method
- Propagation, implication and justification procedures
- D-algorithm
- 9-V algorithm (multiple path sensitization)

General Approaches

- Systematic (algorithmic)
 - Fault table analysis
 - Boolean difference method
 - Fault-oriented methods (D-algorithm, PODEM)
 - Fault-independent methods (critical path tracing)
- Exhaustive/pseudoexhaustive
- Random/pseudorandom


ECE 538

Krish Chakrabarty

3

Fault Table Analysis

2-input OR gate

 

| | | Fault | | | | | |
|------|----|-------|-----|-----|-----|-----|-----|
| | | a/0 | a/1 | b/0 | b/1 | z/0 | z/1 |
| Test | ab | | | | | | |
| | 00 | | x | | x | | x |
| | 01 | | | x | | x | |
| | 10 | x | | | | x | |
| | 11 | | | | | x | |

- Determine fault table via simulation and solve covering problem
- Covering problems are NP-complete
- Computationally infeasible

ECE 538

Krish Chakrabarty

4

Fault-Oriented ATPG

```
Procedure Generate_Tests()  
begin  
  repeat  
    begin  
      Select uncovered fault f  
      Generate test for f  
      Evaluate current fault coverage  
    end  
  until fault coverage > limit, or time runs out  
end
```

Boolean Difference

The Boolean difference of $F(x_1, x_2, x_3, \dots, x_n)$ with respect to x_i is given by

$$\frac{\partial F}{\partial x_i} = F(x_1, x_2, \dots, 1, x_3, \dots, x_n) \oplus F(x_1, x_2, \dots, 0, x_3, \dots, x_n)$$


Cofactor w.r.t. x_i Cofactor w.r.t. \bar{x}_i

Boolean difference provides input combination for sensitized path

A test pattern for $x_i/0$ is an input combination that makes $x_i \frac{\partial F}{\partial x_i} = 1$

A test pattern for $x_i/1$ is an input combination that makes $\bar{x}_i \frac{\partial F}{\partial x_i} = 1$

Boolean Difference

 

To find a test for a/0 or a/1, determine the Boolean difference of output z with respect to a:

$$\frac{\partial z}{\partial a} = ?$$

How to handle internal faults, e.g. j/0?

Key Terminology

- *Backtrace*: move a goal value backwards in a circuit to a primary input
- *Backtrack*: return to a previous decision point in an algorithm and make an alternative decision
- *D-frontier*: Set of gates closest to primary output with D or \bar{D} on some input
- *Implication*: Determine unique signal values that are forced by signal values already assigned
- *Justification*: Determine values to unspecified inputs of gates whose outputs are specified (backward)
- *Propagation (D-drive)*: Determine path values needed to propagate an error signal to a primary output (forward)

Testing Fanout-Free Circuits

- No (reconvergent) fanout
 - Propagation path from any line is unique
 - Each line justification problem is independent of all others

Test generation for line l/v in a fanout-free circuit


```
begin  
  set all values to X (unknown)  
  Justify( $l, \bar{v}$ )  
  if  $v = 0$  then Propagate( $l, D$ )  
  else Propagate( $l, \bar{D}$ )  
end
```

Testing Fanout-Free Circuits

Error propagation:

```
Propagate( $l, err$ )  
/*  $err$  is  $D$  or  $\bar{D}$  */
```
 
```
begin  
  set  $l$  to  $err$   
  if  $l$  is PO then return  
   $k$  = the fanout gate of  $l$   
   $c$  = controlling value of  $k$   
   $i$  = inversion of  $k$   
  for every input  $j$  of  $k$  other than  $l$   
    Justify( $j, \bar{c}$ )  
  Propagate( $k, err \oplus i$ )  
end
```





Testing Fanout-Free Circuits

Justify(l, val)

Line Justification
  
```
begin
  set l to val
  if l is PI then return
  /* l is a gate (output) */
  c = controlling value of l
  i = inversion of l
  inval = val  $\oplus$  i
  if(inval =  $\bar{c}$ )
    then for every input j of l
      Justify(j, inval)
    else
      begin
        Select one input (j) of l
        Justify(j, inval)
      end
  end
```




Functional vs Structural Testing

- Functional ATPG – generate complete set of tests for circuit input-output combinations
 - 129 inputs, 65 outputs:
 - 2^{129} patterns
 - Using 1 GHz ATE, would take 2.15×10^{22} years
- Structural test:
 - No redundant adder hardware, 64 bit slices
 - Each with 27 faults (using fault equivalence)
 - At most $64 \times 27 = 1728$ faults (tests)
 - Takes 0.000001728 s on 1 GHz ATE
- Designer gives small set of functional tests – augment with structural tests to boost coverage to 98+ %

Algorithm Completeness


- Definition: Algorithm is *complete* if it ultimately can search entire binary decision tree, as needed, to generate a test
- *Untestable fault* – no test for it even after entire tree searched
- Combinational circuits only – untestable faults are *redundant*, showing the presence of unnecessary hardware

D-Algorithm

 


| Decision | Implication | Comment |
|---------------|-----------------------------|-----------------|
| $B = \bar{D}$ | $E = \bar{D}, A = 0, a = 0$ | Activate fault |
| $b = 1$ | $C = \bar{D}$ | Propagate via C |
| $F = 0$ | $z = D$ | End of D-drive |
| $H = 0$ | $e = 0$ | Justify F |
| $c = 0 (1)$ | <i>Test: abce = 0100</i> | Justify A |

D-Algorithm

 

| Decision | Implication | Comment |
|--------------------------|-----------------------------|-----------------|
| $B = \bar{D}$ | $E = \bar{D}, A = 0, a = 0$ | Activate fault |
| $H = 1$ | $F = \bar{D}$ | Propagate via F |
| $C = 0$ | $z = D$ | End of D-drive |
| $b = 0$ | $e = 0$ | Justify C |
| $c = 0$ or $e = 0$ | | Justify A |
| <i>Test: abce = 0000</i> | | |

D-Algorithm

 

Single path sensitization does not always work!

| Decision | Implication | Action |
|----------------|---------------------------------------|---|
| $e = D, c = 0$ | $i = \bar{D}, f = 1, h = 0$ | Activate fault, propagate via i |
| $j = k = 0$ | $z = D$ | End of D-drive |
| $d = 1, b = 1$ | $g = 0, e = 0$ ← <i>Contradiction</i> | Justify $j = 0, k = 0$ (<i>Backtrack</i>) |
| $c = 0, d = 0$ | $i = j = \bar{D}$ | propagate through <u>i and j</u> |

Comments on the D-Algorithm


- Based on propagation (primary procedure), justification and implication
- In complete form, guarantees test generation but may require multiple path sensitization (computationally expensive)
- Practical restrictions:
 - Single path sensitization only
 - Limits placed on backtracking time (aborted faults)

9-V Algorithm

- Nine logic values, specified as good/bad pairs: 1/1, 0/0, 1/0, 0/1, u/u, 1/u, 0/u, u/0, u/1
- Example of logic operations: $D.X = 1/0.u/u = u/0$, i.e. provides more information than the X outcome for 5-valued algebra
- Reduces backtracking
 - When there are k possible paths for error propagation, D-algorithm may try all 2^k-1 combinations of paths
 - 9-V enumerates only k ways of propagation

Path Sensitization

- 1 Fault Sensitization
- 2 Fault Propagation
- 3 Line Justification

 


ECE 538

Krish Chakrabarty

19

Path Sensitization

- Try path $f-h-k-L$ blocked at j , since there is no way to justify the 1 on i

 


ECE 538

Krish Chakrabarty

20

Path Sensitization

- Try simultaneous paths $f-h-k-L$ and $g-i-j-k-L$ blocked at k because D -frontier (chain of D or \overline{D}) disappears

 


ECE 538

Krish Chakrabarty

21

Path Sensitization

- Final try: path $g-i-j-k-L$ – test found!

 

ECE 538

Krish Chakrabarty

22

Random Test Generation

- Flow chart for method
- Use to get tests for 60-80% of faults, then switch to D-algorithm or other ATPG for rest

