

ECE 152 Introduction to Computer Architecture


Processor Design: Datapath and Control
Copyright 2012 Daniel J. Sorin
Duke University

Slides are derived from work by
Amir Roth (Penn)
Spring 2012

Where We Are in This Course Right Now

- So far:
 - We know what a computer architecture is
 - We know what kinds of instructions it might execute
 - We know how to perform arithmetic and logic in an ALU
- **Now:**
 - We learn how to design a processor in which the ALU is just one component
 - Processor must be able to fetch instructions, decode them, and execute them
 - There are many ways to do this, even for a given ISA
- **Next:**
 - We learn how to use pipelining to get better performance out of this processor

This Unit: Processor Design

 

- **Datapath components and timing**
 - Registers and register files
 - Memories (RAMs)
- Mapping an ISA to a datapath
- Control
- Exceptions


Readings

- Patterson and Hennessy
 - Chapter 4: Sections 4.1-4.4
- Read this chapter carefully
 - It has many more examples than I can cover in class

So You Have an ALU...

- **Important reminder:** a processor is just a big finite state machine (FSM) that interprets some ISA
- Start with one instruction
 - `add $3,$2,$4`
 - ALU performs just a small part of execution of instruction
 - You have to read and write registers
 - You have to fetch the instruction to begin with
- What about loads and stores?
 - Need some sort of memory interface
- What about branches?
 - Need some hardware for that, too

Datapath and Control

 

- **Datapath:** registers, memories, ALUs (computation)
- **Control:** which registers read/write, which ALU operation
- **Fetch:** get instruction, translate into control
- Processor Cycle: **Fetch** → **Decode** → **Execute**

Building a Processor for an ISA


- Fetch is pretty straightforward
 - Just need a register (called the Program Counter or PC) to hold the next address to fetch from instruction memory
 - Provide address to instruction memory → instruction memory provides instruction at that address
- Let's start with the datapath
 1. Look at ISA
 2. Make sure datapath can implement every instruction

Datapath for MIPS ISA

- Consider only the following instructions


```
add $1,$2,$3
addi $1,2,$3
lw $1,4($3)
sw $1,4($3)
beq $1,$2,PC_relative_target
j Absolute_target
```
- Why only these?
 - Most other instructions are similar from datapath viewpoint
 - I leave the other ones for you to figure out

 Review (ECE 52 & Project Part1): Register




- **Register:** DFF array with shared clock, write-enable (WE)
 - Notice: both a clock and a WE ($DFF_{WE} = \text{clock} \& \text{register}_{WE}$)
 - Convention I: clock represented by wedge
 - Convention II: if no WE, DFF is written on every clock

Uses of Registers

 


- A single register is good for some things
 - PC: program counter
 - Other things which aren't the ISA registers
 - ICQ: other examples from within the ALU, mult, div?

What About the ISA Registers?

 


- **Register file:** the ISA ("architectural", "visible") registers
 - Two read "ports" + one write "port"
 - Maximum number of reads/writes in single instruction (R-type)
- **Port:** wires for accessing an array of data
 - Data bus: width of data element (MIPS: 32 bits)
 - Address bus: width of \log_2 number of elements (MIPS: 5 bits)
 - Write enable: if it's a write port
 - M ports = M parallel and independent accesses

A Register File With Four Registers

 


Add a Read Port for RS1

 


- Output of each register into 4to1 mux (RS1VAL)
 - RS1 is select input of RS1VAL mux

Add Another Read Port for RS2

 

- Output of each register into another 4to1 mux (RS2VAL)
 - RS2 is select input of RS2VAL mux

Add a Write Port for RD

 


- Input RDVAL into each register
 - Enable only one register's WE: (Decoded RD) & (WE)
- What if we needed two write ports?


Another Read Port Implementation

- A read port that uses muxes is fine for 4 registers
 - Not so good for 32 registers (32-to-1 mux is very slow)
- Alternative implementation uses **tri-state buffers**
 - Truth table (E = enable, D = input, Q = output)


E	D	Q
1	D	D
0	D	Z
 - **Z**: "high impedance" state, no current flowing
- Mux: connect multiple tri-stated buses to one output bus
- Key: only one input "driving" at any time, all others must be in "Z"
 - Else, all hell breaks loose (electrically)

 

Register File With Tri-State Read Ports

 


Another Useful Component: Memory

 

- **Memory**: where instructions and data reside
 - One read/write "port": one access per cycle, either read **or** write
 - One address bus
 - One input data bus for writes, one output data bus for reads


Let's Build A MIPS-like Datapath

Start With Fetch

 

- PC and instruction memory
- A +4 incrementer computes default next instruction PC
 - Why +4 (and not +1)? What will it be for 32-bit Duke 152/32?

First Instruction: add \$rd, \$rs, \$rt

 

- Add register file and ALU