

ECE 254 / CPS 225
Fault Tolerant and Testable Computing Systems

Testing and Design for Test

Copyright 2011 Daniel J. Sorin
Duke University

Outline

- **Introduction and Terminology**
- **Test Generation for Single Stuck-At Faults**
- **Functional Testing**
- **Software Testing**
- **Design For Test (DFT)**
- **Built-In Self-Test (BIST)**

A Good Reference and a Caveat

- M. Abramovici, M. Breuer, and A. Friedman. "Digital Systems Testing and Testable Design", IEEE Press, 1990.
- This book is the basis for much of the material in this section of the course, but many other textbooks on this subject exist.
- **Caveat: ECE 254 is not a course on testing and testable systems. This course only has a small segment on these topics. If you're interested in pursuing this topic further, there are classes and research in ECE that you should explore.**
 - See Prof. Chakrabarty (ECE 269)

Testing

- **Testing: applying inputs to system and comparing outputs to expected outputs (for given inputs)**
 - Goal: detect hard faults in system
 - Example: you drive a used Toyota Corolla before buying it
- **(static, offline) Verification: checking the system design to make sure that it meets the specification**
 - Goal: detect design flaws
 - Example: Toyota ensures that Corolla design will get 45 mpg
- **Caveat: a verified design can be manufactured into a system that doesn't work correctly due to a flaw in manufacturing**
 - This is why we need testing!
 - Example: Toyota makes 2% of Corollas that get only 30 mpg


Aside on Dynamic Verification

- Normally, when we talk about verification, we are referring to static verification (as in previous slide)
- New terminology: **dynamic verification** = checking the behavior of a system as it is running
 - This is a form of error detection that operates at a higher level by checking higher level invariants of system behavior
 - E.g., DIVA is a dynamic verification scheme for microprocessor
 - Can detect operational faults
 - Can detect design faults
- Dynamic verification is known as **online testing** or **concurrent testing** in the testing research community

Testing Hardware and Software


- Can test hardware and/or software
- Why test hardware?
 - Detect manufacturing faults
 - Can catch some design faults that were missed by verification
 - » Verification is not perfect for large complicated systems!
- Why test software?
 - Detect design faults (bugs) that were missed by verification
 - » Verification is very imperfect for real software
- For both, we apply inputs to the system and compare the outputs to what we expect for the given inputs
- For now, we focus on low-level hardware testing ... and we start with combinational logic only

Testing Example

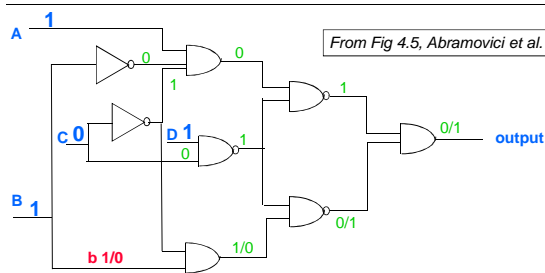

- Test vector **ABCD=1101** detects fault **b stuck-at-0**
 - Question for later: do you see any other tests that detect this fault?
 - » Hint: does value of D matter?

Fault Activation

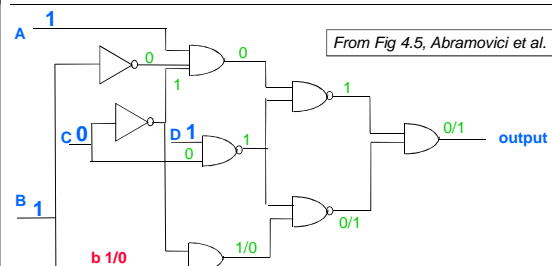

- This test (**ABCD=1101**) **activates** the fault **b stuck-at-0**
 - Generates an error at the site of the fault
 - Line **justification** problem: choosing a set of input values that puts a desired value on a given line in the circuit

Error Propagation

From Fig 4.5, Abramovici et al.

- This test **propagates** the error to a primary output
 - Makes all the lines along at least one path from fault site to output have different values in the presence of the fault

(C) 2011 Daniel J. Sorin ECE 254 / CPS 225 9

Sensitization (yes, this is a word)

From Fig 4.5, Abramovici et al.

- During the test, all lines whose values change in the presence of the fault are **sensitized**
 - A path of sensitized lines is a **sensitized path**

(C) 2011 Daniel J. Sorin ECE 254 / CPS 225 10

Detectability

- We want to choose inputs that test for all faults
 - Goal: smallest set of test vectors that **covers** all **detectable** faults
 - Do not necessarily need 2^N vectors for N-input circuit
- Some faults are undetectable
 - Due to redundancy in circuit, the faults are **masked**
 - So then why care about them? (Hint: single fault assumption)
- Simple example: TMR
 - How could you test for a fault in one replica?
 - Would have to add circuitry to be able to test them individually

(C) 2011 Daniel J. Sorin ECE 254 / CPS 225 11

Why Undetectable Faults Are Bad

From Fig 4.5, Abramovici et al.

- Test vector **ABCD=1101** does **NOT** detect **b stuck-at-0** if undetectable fault **a stuck-at-1** is present

(C) 2011 Daniel J. Sorin ECE 254 / CPS 225 12

Functional Equivalence of Faults

- Two faults are functionally equivalent if the output is the same in the presence of each
- Simple example: NOT gate
 - Input stuck-at-0 is equivalent to output stuck-at-1


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

13

Functional Equivalence Example

From Fig 4.11, Abramovici et al.

 

- Bridging fault between A and B is functionally equivalent to output stuck-at-0


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

14

Functional Equivalence Example

From Fig 4.11, Abramovici et al.

 

- Bridging fault between A and B is functionally equivalent to output stuck-at-0
 - Consider case where A would've been 0 but now stuck at 1


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

15

Functional Equivalence Example

From Fig 4.11, Abramovici et al.

 

- Bridging fault between A and B is functionally equivalent to output stuck-at-0
 - Consider case where A would've been 1 but now stuck at 0


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

16

Fault Collapsing

- If a set of faults is functionally equivalent, we only need to use one test to detect any single one of them
 - Reducing the set of faults to test for by using equivalence classes is called **fault collapsing**
- Note that a test that detects functionally equivalent faults cannot diagnose which fault is present
 - To test for fault location requires distinguishable faults
- Simple example: 2-input NAND gate

 


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

17

Fault Collapsing

- If a set of faults is functionally equivalent, we only need to use one test to detect any single one of them
 - Reducing the set of faults to test for by using equivalence classes is called **fault collapsing**
- Note that a test that detects functionally equivalent faults cannot diagnose which fault is present
 - To test for fault location requires distinguishable faults
- Simple example: 2-input NAND
 - Input stuck-at-0 is equivalent to output stuck-at-1 → collapse!

 


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

18

Fault Dominance

 - A fault **f dominates** a fault **g** if any test that detects **g** also detects **f** (on the same output)
 - We don't have to test for the dominating fault **f**, since any test for **g** will test for **f**
- Back to our simple NAND example (after collapsing equivalent faults)




(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

19

Fault Dominance

- A fault **f dominates** a fault **g** if any test that detects **g** also detects **f** (on the same output)
 - We don't have to test for the dominating fault **f**, since any test for **g** will test for **f**
- Back to our simple NAND example (after collapsing equivalent faults)
 - Test input vector to detect input B stuck-at-1 is $AB=10$, which also detects if the output is stuck-at-0. Thus, output stuck-at-0 dominates B stuck-at-1 and we don't need to test for it.
 - This reduction is called **dominance fault collapsing**

 

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

20

Outline

- Introduction and Terminology
- **Test Generation for Single Stuck-At Faults**
- Functional Testing
- Software Testing
- Design For Test (DFT)
- Built-In Self-Test (BIST)

Test Generation for Single Stuck-Ats

- **Types of test generation (TG)**
 - Random
 - Deterministic
 - » Manual
 - » Automatic
 - Hybrids of random and deterministic
- **Goals**
 - Quick, low-complexity process for generating faults
 - High fault coverage
 - Small number of test vectors

Random Test Generation

- **Randomly produce test vectors**
- **Advantages**
 - Easy and fast generation of test vectors
 - Can easily detect lots of faults with random tests
- **Disadvantages**
 - May take a huge set of test vectors to cover the hard-to-detect faults (i.e., faults that are only activated by a small number of possible tests)

Deterministic Test Generation

- **Can develop test vectors to target specific faults**
 - Particularly useful for hard-to-detect faults
 - Manual test generation is not feasible for large circuits
- **Automatic test generation (ATG) uses algorithms to devise tests that:**
 - Activate each fault
 - Propagate the resulting error to an output
- **After generating a set of tests for every fault, then ATG collapses the test set as much as possible**
 - Functional equivalence
 - Fault dominance

Hybrid Testing


- **Goal: achieve best of both worlds**
 - Random: low cost, quick generation of test vectors
 - Deterministic: smaller test vector sets
- **Use random TG to quickly cover most faults**
- **Use deterministic ATG to cover the hard-to-detect faults**

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

25

Example of Activation and Propagation

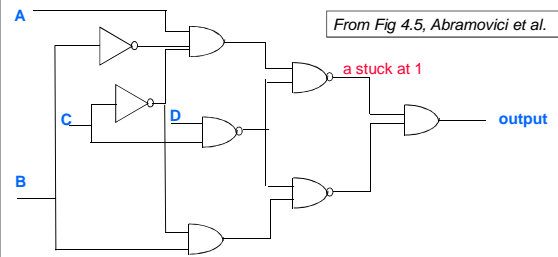


- **To test for a stuck-at-1, we must activate it and propagate it**

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

26

Example of Activation and Propagation

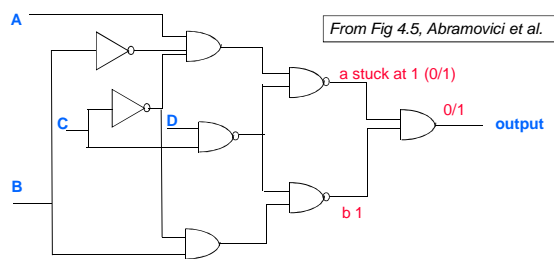


- **To propagate it, must set b to 1**
 - Otherwise, the output would always be 0
 - Output is now equal to a (i.e., output = 0/1)

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

27

Example of Activation and Propagation

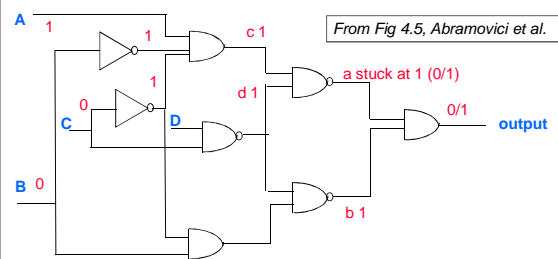


- **We must set a=0, and this implies that both of its inputs must be 1, which implies that A=1, B=0, and C=0**

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

28

Example of Activation and Propagation

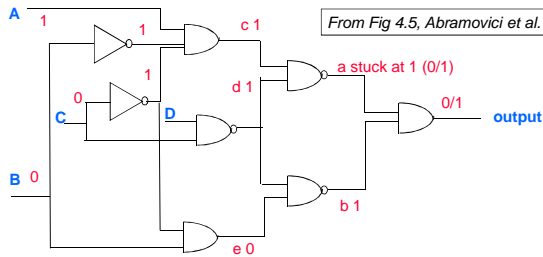


- B=0 implies that e=0, which implies that b=1 (whew!)
- Note that C=0 implies that d=1 (also good)

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

29

Example of Activation and Propagation

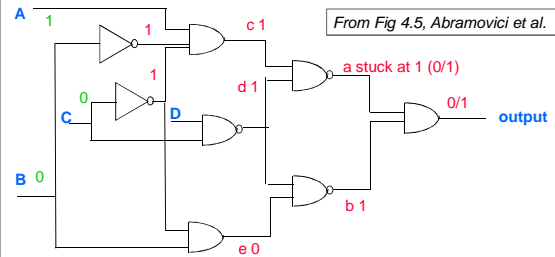

- So now we've determined that our test is ABCD=100x
– The value of D doesn't matter for this test


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

30

Implication

 - We lucked out in the previous example --- we never implied a value on a line that was incompatible with another implicated value for that line
- If that happened, we'd have to try to find another test
- Example below: a stuck-at-1
– Implicated values shown in green ... so far, so good




(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

31

Implication

 - We lucked out in the previous example --- we never implied a value on a line that was incompatible with another implicated value for that line
- If that happened, we'd have to try to find another test
- Example below: a stuck-at-1
– We now have that A=1 and B=1, but A and B = 1 → backtrack!




(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

32

ATG for Sequential Circuits

 - So far, we've only looked at combinational logic
- How can we deal with sequential logic?
- One option: make it look more like combinational!
 - Make each cycle a new **frame** of a combinational circuit




(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

33

ATG for Sequential Circuits

 - So far, we've only looked at combinational logic
- How can we deal with sequential logic?
- One option: make it look more like combinational!
 - Make each cycle a new **frame** of a combinational circuit




(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

34

ATG for Sequential Circuits

 - Now, we want to be able to propagate an error to an output $Z(n)$, where smaller n is better (quicker!)
- The test sequence is $X(0), X(1), \dots, X(n)$
 - Remember that each $X(i)$ is a test vector of inputs (at cycle i)




(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

35

ATG for Sequential Circuits

 - Using time frames, we can create a combinational circuit and then just use ATG for combo circuits
- Catch: have to choose **when** to propagate fault, i.e., must choose n for $Z(n)$. If impossible, try larger n



(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

36

Outline

- Introduction and Terminology
- Test Generation for Single Stuck-At Faults
- **Functional Testing**
- Software Testing
- Design For Test (DFT)
- Built-In Self-Test (BIST)

Functional Testing

- **Testing a system at a higher level of abstraction**
 - If a system works at higher level, then you don't have to worry about the lower level
 - The user only sees the high level abstraction, not transistors
- **For example, instead of testing for every possible stuck-at in a Pentium4, test to see if it boots Windows**
 - If it boots Windows, you might believe that it is OK
- **Other examples?**

- **Functional testing can be done at many levels**
 - E.g., you could probably consider stuck-at testing to be functional if you were only worried about logic gate functionality

Why Use Anything BUT Functional Testing?

- If functional testing subsumes lower-level testing, why do we bother with low level testing for stuck-ats?
- **Reason #1: Devising functional tests with good fault coverage isn't easy**
- **Reason #2: Fault location and diagnosis --- during fabrication, if you notice that a lot of faults are in the same place, you might be able to adjust the fabrication process to make that place less of a problem**
- **Any other reasons?**

Validation in the Real World

"Validating the Pentium 4 Microprocessor," by Bob Bentley and Rand Gray (Intel), DSN 2001

Outline

- Introduction and Terminology
- Test Generation for Single Stuck-At Faults
- Functional Testing
- **Software Testing**
- Design For Test (DFT)
- Built-In Self-Test (BIST)

Software Testing

- **Goal: stress-test the software in order to find bugs more quickly than would occur for typical inputs**
- **This is a job that many entry-level software engineers start with**
 - Trying to break software forces engineer to better understand it
- **Software testing tends to be almost entirely functional testing**

When Do We Stop Testing?

- **Comprehensive software testing is impossible problem for almost all real software**
 - Must try to find as many bugs as possible, while realizing that it's impossible to find all of them
- **So when do we stop testing?**
 - When rate of bug detection decreases below threshold
- **Threshold depends on software**
 - People rely more on Microsoft Windows than they do on a small utility program → Microsoft *should* test more thoroughly
- **Key idea: if you're still finding lots of bugs, it's likely that there are still a bunch more that you haven't found yet**

Software Testing Techniques

- **Test software in parallel**
 - Get many people to test it for you → release a beta test version of cool software and people will test it for free
 - » This is how I helped to debug a simulator called Simics
- **Provide software with worst-case or unusual inputs**
 - Input a number when prompted for a string
 - Input a character when asked for a floating point number
 - When asked how many entries you'll need in a database, give it a huge number and see if that breaks it (e.g., because the database stupidly tries to allocate all that memory immediately)
 - When configuring a simulator, give it unusual parameters
 - Etc.

Testing Non-deterministic Software

- **Non-determinism**: if a program won't behave the same exact way each time it is run with the same inputs
- **With non-determinism, it is very hard to reproduce a bug, so a test that finds it once may not be able to find it again**
 - You may not be able to tell the programmers what to fix

Outline

- Introduction and Terminology
- Test Generation for Single Stuck-At Faults
- Functional Testing
- Software Testing
- **Design For Test (DFT)**
- Built-In Self-Test (BIST)


Design for Test (DFT)

- **How do we design a system so that it has good testability?**
- **We must improve the system's:**
 - **Controllability**: ability to control the value of lines in the circuit
 - » 1-controllability: ability to set line to 1
 - » 0-controllability: ability to set line to 0
 - **Observability**: ability to observe the values of lines in the circuit
- **We're going to cover two classes of approaches**
 - Ad hoc schemes
 - Systematic schemes that use scan registers

Ad Hoc Scheme 1: Test Points

- **We can add test points to the circuit**
 - Control points
 - Observation points
- **Control points are added inputs that we use to improve controllability**
- **Observation points are added outputs that we use to improve observability**

Control Point Example

 


- Adding new input C enables us to better control line X
 - Can easily set X to 1 (by setting C to 0)

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

49

Observation Point Example

 

- Adding new output D enables us to easily observe line Y

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

50

Ad Hoc Scheme 2: Initialization

- For sequential circuits, it is important to be able to get the circuit into a known state
 - It's tough to test something that's in an unknown state


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

51

Ad Hoc Scheme 3: Partitioning

 - For large circuits or circuits with many states, it is easier to test them if we break them up into smaller sub-circuits
 - As functions of circuit size, testing time and complexity are greater than linear
- In general, we can partition circuits by adding multiplexor logic and new controllability inputs:



(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

52

Ad Hoc Scheme 4: Avoiding Redundancy

- Recall that redundancy in circuits can lead to undetectable faults
- Two types of redundancy
 - Intentional: used for fault tolerance (good!)
 - Unintentional: most circuits have redundancy unless they've been optimized specifically to eliminate it (not good)
- We'd like to get rid of unintentional redundancy
- We'd like to keep intentional redundancy, but this means that we'll need to add test points to make sure that we can detect faults in the redundant logic


(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

53

Systematic DFT: Scan Registers

 - Test points are great, but they add lots of pins to a chip (both for inputs and outputs)
 - Pins are an expensive, scarce resource




(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

54

Systematic DFT: Scan Registers

 - One way to add test points without adding so many pins is to use **scan registers** (shift registers)
 - Sequentially scan test vector into scan register via a single pin, and then apply shift register contents to control points
 - Similarly, scan observation points into scan register and read out sequentially via a single pin



(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

55

Scan Registers

- **Advantage**
 - Fewer pins!
- **Disadvantages**
 - Need scan hardware
 - Sequential → slower!!
- **Commercial chips have scan registers**
 - JTAG and IEEE standards for scan register design
- **There are many, many different types of scan registers and scan design methodologies, but we will not cover these in this course**

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

56

Outline

- Introduction and Terminology
- Test Generation for Single Stuck-At Faults
- Functional Testing
- Software Testing
- Design For Test (DFT)
- Built-In Self-Test (BIST)

Goals of BIST

- Want system to be able to test itself
- Why?
 - Generation of test vectors within chip eliminates pins used for testing → cheaper and higher bandwidth
 - Enables in-field testing (after deployment)
 - » If hard fault detected, can notify user and/or reconfigure system to handle the fault

Off-line vs. Online BIST


- Off-line
 - Testing while system is not performing its normal functions
- On-line or concurrent
 - Testing during operation
 - Also known as **dynamic verification**

A Paradox?

- If the system uses its own BIST hardware to test itself, how does it test this BIST hardware?
- Must be able to boot-strap based on assumption that a certain amount of the system (called the **hardcore**, for reasons I can't explain) is operational
 - Remember this concept from the Teramac paper??
- Examples of hardcore circuitry
 - Power and ground
 - Clock distribution
 - Test generation logic
- Probably need to do external testing to determine if hardcore is faulty

Hardware for Generating Pseudo-Random Tests

 - **Linear feedback shift register (LFSR)**
 - Shift register with XOR-based feedback loop
 - C_i are feedback coefficients
 - $C_i=1$ implies that a connection exists
- Based on initial state and choice of C_i , LFSR can generate long pseudo-random sequences (up to 2^n-1 , where n is number of stages in LFSR)



(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

61

Flavors of BIST

- **Exhaustive**
 - Generate and apply all 2^n possible input combinations
- **Pseudo-random**
 - Similar to random ATG, but tests generated with LFSRs
- **Pseudo-exhaustive**
 - Partitions system and exhaustively tests these smaller sub-circuits

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

62

Outline

- Introduction and Terminology
- Test Generation for Single Stuck-At Faults
- Functional Testing
- Software Testing
- Design For Test (DFT)
- Built-In Self-Test (BIST)

(C) 2011 Daniel J. Sorin

ECE 254 / CPS 225

63