

Decimal Multiplication

- Remember decimal multiplication from 3rd grade?

```

  43 // multiplicand
* 12 // multiplier
  86
+ 430
 516 // product
    
```

- Start with running total 0, repeat steps until no multiplier digits
 - Multiply multiplicand by least significant multiplier digit
 - Add to total
 - Shift multiplicand one digit to the left (multiply by 10)
 - Shift multiplier one digit to the right (divide by 10)
- Product of N-digit and M-digit numbers potentially has N+M digits


Binary Multiplication

```

  43 = 00000101011 // multiplicand
* 12 = 00000001100 // multiplier
  0 = 00000000000
  0 = 00000000000
 172 = 00010101100
+ 344 = 00101011000
 516 = 01000000100 // product
    
```


- Same thing except ...
 - There are more individual steps (smaller base)
 - But each step is simpler
 - Multiply multiplicand by **least significant multiplier bit**
 - 0 or 1 → no actual multiplication, just add multiplicand or not
 - Add to total: we know how to do that
 - Shift multiplicand left, multiplier right by one bit: **shift registers**

Simple 16x16=32bit Multiplier Circuit

 


- Control algorithm:** repeat 16 times
 - If LSB(multiplier) == 1, then add multiplicand to product
 - Shift multiplicand left by 1
 - Shift multiplier right by 1

Inefficiencies with Simple Circuit

 

- Notice
 - 32-bit addition, but 16 multiplicand bits are always 0
 - And 0 bits are always moving
 - Solution? Instead of shifting multiplicand left, shift product right


Better 16-bit Multiplier

 

4b example:
0101 x 0110


- **Control algorithm:** repeat 16 times
 - LSB(multiplier) == 1 ? Add multiplicand to upper half of product
 - Shift multiplier right by 1
 - Shift product right by 1

Another Inefficiency

 

- Notice one more inefficiency
 - What is initially the lower half of product gets thrown out
 - As useless lower half of product is shifted right, so is multiplier
 - Solution: use lower half of product as multiplier

Even Better 16-bit Multiplier

 

4b example:
0101 x 0110

- **Control algorithm:** repeat 16 times
 - LSB(multiplier) == 1 ? Add multiplicand to upper half of product
 - Shift product right by 1

Multiplying Negative Numbers

- Just works...
 - As long as right shifts are arithmetic and not logical
 - Try it out for yourself now
- $0101 * 1111 = ?$

Booth's Algorithm

- Notice the following equality (Booth did)
 - $2^j + 2^{j-1} + 2^{j-2} + \dots + 2^k = 2^{j+1} - 2^k$
 - Example: $0111 = 1000 - 0001$
 - We can exploit this to create a faster multiplier
- How?
 - Sequence of N 1s in the multiplier yields sequence of N additions
 - Replace with one addition and one subtraction

Booth In Action


- For each multiplier bit, also examine bit to its right
 - 00**: middle of a run of 0s, do nothing
 - 10**: beginning of a run of 1s, subtract multiplicand
 - 11**: middle of a run of 1s, do nothing
 - 01**: end of a run of 1s, add multiplicand

```

43 = 0000101011
* 12 = 0000001100
-----
0 = 0000000000 // multiplier bits 0_ (implicit 0)
+ 0 = 0000000000 // multiplier bits 00
- 172 = 1110101010 // multiplier bits 10
+ 0 = 0000000000 // multiplier bits 11
+ 688 = 0101011000 // multiplier bits 01
-----
516 = 0100000100
    
```

ICQ: so why is Booth better?

Booth Hardware

 

- Control algorithm:** repeat 16 times
 - Multiplier LSBs == 10? Subtract multiplicand from product
 - Multiplier LSBs == 01? Add multiplicand to product
 - Shift product/multiplier right by 1 (not by 2!)

Booth in Summary

- Performance/efficiency
 - + Good for sequences of 3 or more 1s
 - Replaces 3 (or more) adds with 1 add and 1 subtract
 - Doesn't matter for sequences of 2 1s
 - Replaces 2 adds with 1 add and 1 subtract (add = subtract)
 - Actually bad for singleton 1s
 - Replaces 1 add with 1 add and 1 subtract
- Bottom line
 - Worst case multiplier (101010) requires $N/2$ adds + $N/2$ subs
 - What is the worst case multiplier for straight multiplication?
 - How is this better than normal multiplication?

Modified Booth's Algorithm


- What if we detect singleton 1s and do the right thing?
- Examine multiplier bits in groups of 2s plus a helper bit on the right (as opposed to 1 bit plus helper bit on right)
 - Means we'll need to shift product/multiplier by 2 (not 1)
- **000**: middle of run of 0s, do nothing
- **100**: beginning of run of 1s, subtract multiplicand $\ll 1$ ($M \cdot 2$)
 - Why $M \cdot 2$ instead of M ?
- **010**: singleton 1, add multiplicand
- **110**: beginning of run of 1s, subtract multiplicand
- **001**: end of run of 1s, add multiplicand
- **101**: end of run of 1s, beginning of another, subtract multiplicand
 - Why is this? $-2^{i+1} + 2^i = -2^i$
- **011**: end of a run of 1s, add multiplicand $\ll 1$ ($M \cdot 2$)
- **111**: middle of run of 1s, do nothing

Modified Booth In Action

```


43 = 0000101011
* 12 = 0000001100
-----
0 = 0000000000 // multiplier bits 000
- 172 = 11101010100 // multiplier bits 110
+ 688 = 01010110000 // multiplier bits 001
-----
516 = 01000000100
    
```

Modified Booth Hardware

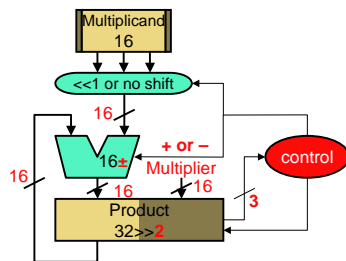

- **Control algorithm**: repeat 8 times
 - Based on 3b groups, add/subtract shifted/unshifted multiplicand
 - Shift product/multiplier right by 2

Another Multiplier: Multiple Adders

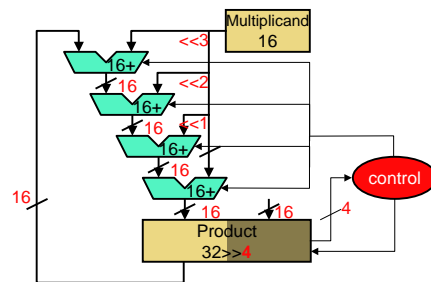


- Can multiply by N bits at a time by using N adders
 - Doesn't help: 4X fewer iterations, each one 4X longer ($4 \cdot 9 = 36$)


Carry Save Addition (CSA)

- **Carry save addition (CSA):** $d(N \text{ adds}) < N * d(1 \text{ add})$
 - Enabling observation: unconventional view of full adder
 - 3 inputs (A,B,C_{in}) → 2 outputs (S,C_{out})
 - If adding two numbers, only thing to do is chain C_{out} to C_{in+1}
 - But what if we are adding three numbers (A+B+D)?
- One option: back-to-back conventional adders
 - (A,B,C_{inT}) → (T,C_{outT}), chain C_{outT} to C_{inT+1}
 - (T,D,C_{inS}) → (S,C_{outS}), chain C_{outS} to C_{inS+1}
- Notice: we have **three independent inputs** to feed first adder
 - (A,B,D) → (T,C_{outT}), **no chaining (CSA: 2 gate levels)**
 - (T,C_{outT},C_{inS}) → (S,C_{outS}), chain C_{outS} to C_{inS+1}

Carry Save Addition (CSA)

 


 - 2 conventional adders
 - $2 * d(\text{add})$ gate levels
 - $d(\text{add}16)=9$
 - → $d = 18$
- k conventional adders
 - $k * d(\text{add})$ gate levels



- CSA+conventional adder
 - $2 + d(\text{add})$ gate levels
 - → $d = 11$
- k CSAs+conventional add
 - $2 + d(\text{add})$ gate levels

Carry Save Multiplier

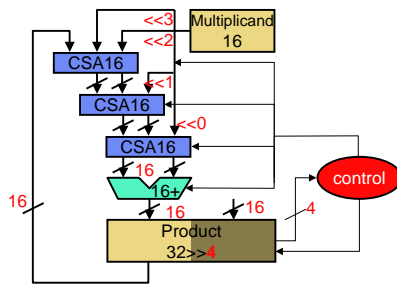

- 4-bit at a time multiplier using 3 CSA + 1 normal adder
 - Actually helps: 4X fewer iterations, each only $(2+2+2+9=15)$