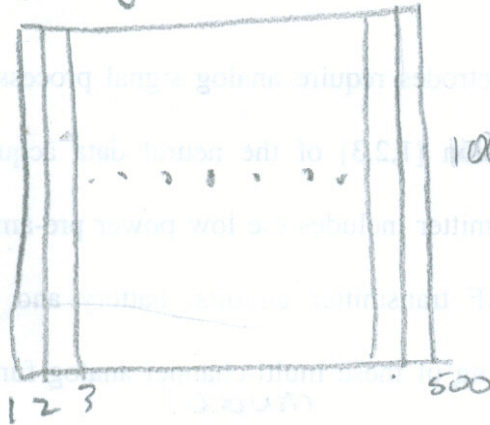


HW 2

1)

ONE LAYER




AS PER ground rule we have  
2 μm metal on center  
∴ 500 lines on 2 μm center

$$\text{length of wire/layer} = 500 \times 10\text{cm} + 1\text{cm} = 501\text{cm/layer}$$

$$\text{Total length} = 8\text{ lay} / 501\text{cm/lay} = 4008\text{cm} = 400.8\text{meters}$$

TOTAL LENGTH  $\approx$  400.8 football fields

2) a) Prob 4.6

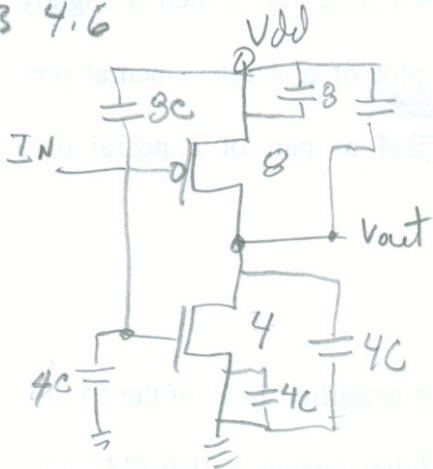

$$C_{in} = 12C$$

$$\text{Logic Effort} = \frac{12C}{12C} = 1$$

PARASITIC DELAY

$$R = \frac{1}{4} R_{inv}$$

$$C = 4 C_{inv}$$

$$\therefore \frac{1}{4} R_{inv} \cdot 4 C_{inv} = R_{inv} C_{inv} = P_{inv}$$

$$\therefore \underline{P = P_{inv}}$$

UNIT INVERTER

