

Arithmetic Circuits-2

- Multipliers
 - Array multipliers
- Shifters
 - Barrel shifter
 - Logarithmic shifter

Binary Multiplication

$$X = \sum_{i=0}^{M-1} X_i 2^i$$

Multiplicand

$$Y = \sum_{i=0}^{N-1} Y_i 2^i$$

Multiplier

Product

$$Z = X * Y$$

$$= \sum_{i=0}^{N-1} \left(\sum_{j=0}^{M-1} X_i Y_j 2^{i+j} \right)$$

Partial products

- Product = Sum of partial products

Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ \underline{0101} : 5_{10} \end{array}$$

Multiplication

- Example:

$$\begin{array}{r} 1100 \\ \times 0101 \\ \hline 1100 \\ \\ \\ 1100 \end{array} \quad \begin{array}{l} : 12_{10} \\ : 5_{10} \end{array}$$

Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ \hline \end{array}$$

Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ \hline \end{array}$$

Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline \end{array}$$

Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 00111100 : 60_{10} \end{array}$$

Multiplication

- Example:

$$\begin{array}{r} 1100 : 12_{10} \\ 0101 : 5_{10} \\ \hline 1100 \\ 0000 \\ 1100 \\ 0000 \\ \hline 00111100 : 60_{10} \end{array}$$

multiplicand
multiplier
partial products
product

- M x N-bit multiplication
 - Produce N M-bit partial products
 - Sum these to produce M+N-bit product

The Binary Multiplication

1 0 1 0 1 0	Multiplicand
1 0 1 1	Multiplier
<hr/>	
1 0 1 0 1 0	AND operation
1 0 1 0 1 0	Partial Products
0 0 0 0 0 0	
+ 1 0 1 0 1 0	
<hr/>	
1 1 1 0 0 1 1 1 0	

General Form


- Multiplicand: $Y = (y_{M-1}, y_{M-2}, \dots, y_1, y_0)$
- Multiplier: $X = (x_{N-1}, x_{N-2}, \dots, x_1, x_0)$

- Product:
$$P = \left(\sum_{j=0}^{M-1} y_j 2^j \right) \left(\sum_{i=0}^{N-1} x_i 2^i \right) = \sum_{i=0}^{N-1} \sum_{j=0}^{M-1} x_i y_j 2^{i+j}$$


					y_5	y_4	y_3	y_2	y_1	y_0	multiplicand multiplier
					x_5	x_4	x_3	x_2	x_1	x_0	
					$x_0 y_5$	$x_0 y_4$	$x_0 y_3$	$x_0 y_2$	$x_0 y_1$	$x_0 y_0$	partial products product
				$x_1 y_5$	$x_1 y_4$	$x_1 y_3$	$x_1 y_2$	$x_1 y_1$	$x_1 y_0$		
			$x_2 y_5$	$x_2 y_4$	$x_2 y_3$	$x_2 y_2$	$x_2 y_1$	$x_2 y_0$			
			$x_3 y_5$	$x_3 y_4$	$x_3 y_3$	$x_3 y_2$	$x_3 y_1$	$x_3 y_0$			
			$x_4 y_5$	$x_4 y_4$	$x_4 y_3$	$x_4 y_2$	$x_4 y_1$	$x_4 y_0$			
			$x_5 y_5$	$x_5 y_4$	$x_5 y_3$	$x_5 y_2$	$x_5 y_1$	$x_5 y_0$			
p_{11}	p_{10}	p_9	p_8	p_7	p_6	p_5	p_4	p_3	p_2	p_1	p_0

Dot Diagram

- Each dot represents a bit

 


The Array Multiplier

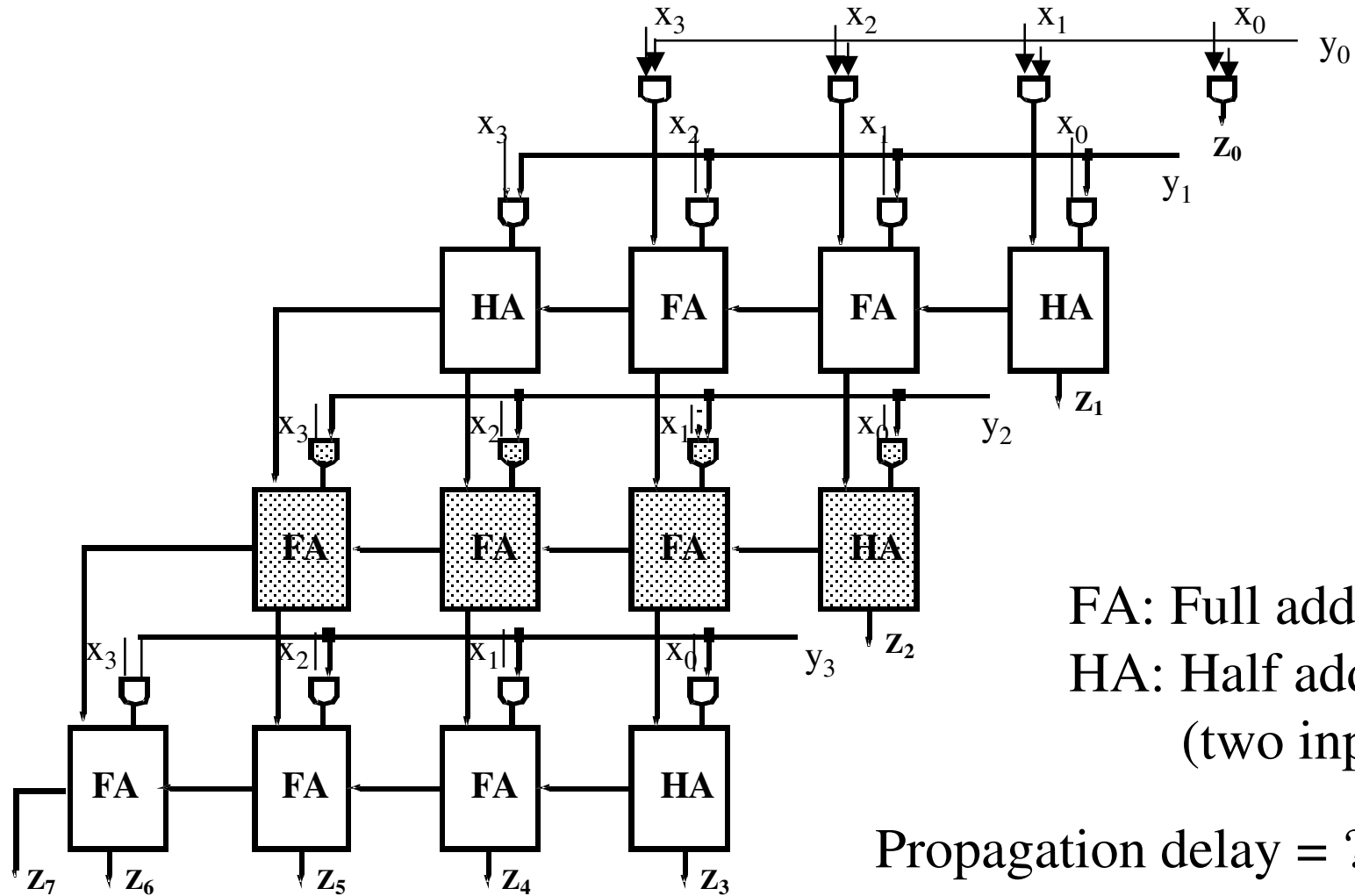


The MxN Array Multiplier

— Critical Path

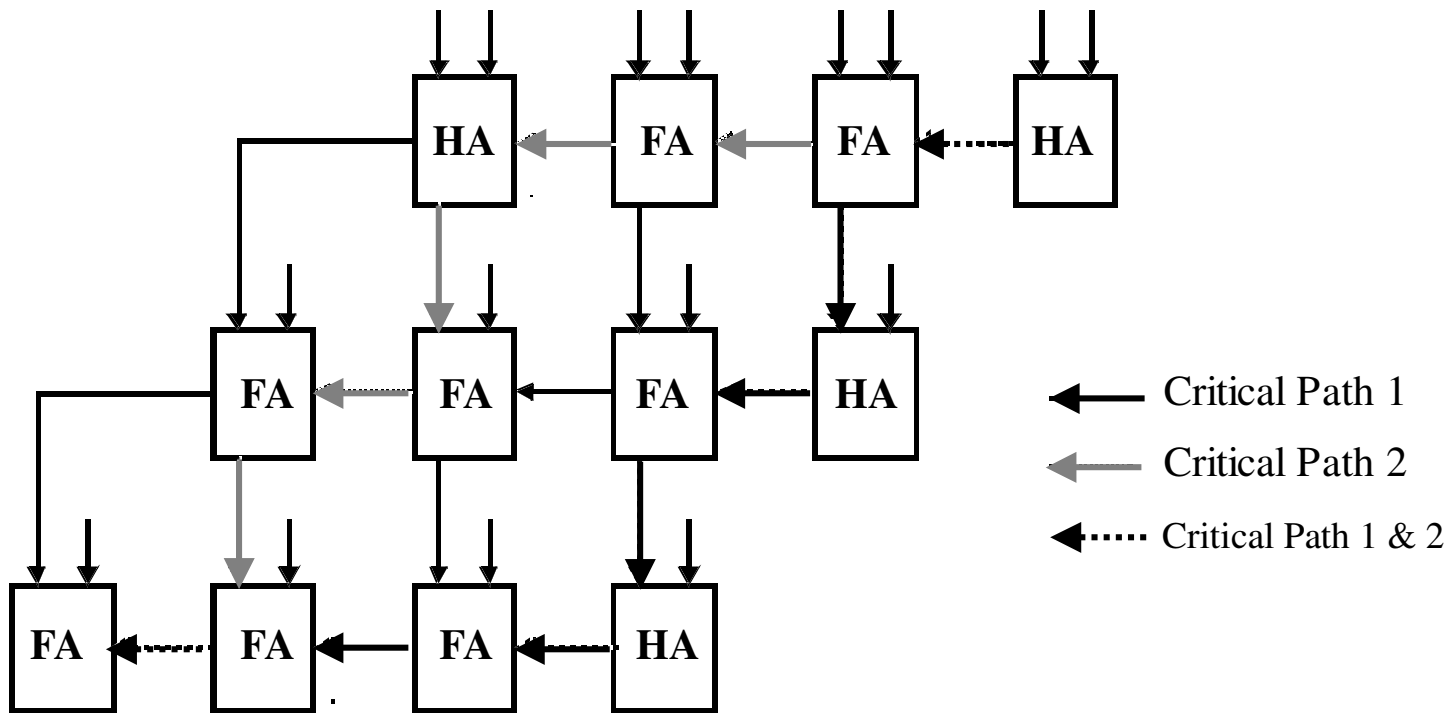

$$t_{mult} \approx [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$

Carry-Save Multiplier

 




Carries saved for next
adder stage

Unique critical path

Trade offs?


$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

Adder Cells in Array Multiplier

   

Identical Delays for Carry and Sum

Multiplier Floorplan

 

Multipliers — Summary




- **Optimization Goals Different Vs Binary Adder**
- **Once Again: Identify Critical Path**
- **Other possible techniques**
 - **Logarithmic versus Linear** (Wallace tree multiplier)
 - **Data encoding (Booth)**
 - **Pipelining**

Comparators

- 0's detector: $A = 00\dots000$
- 1's detector: $A = 11\dots111$
- Equality comparator: $A = B$
- Magnitude comparator: $A < B$


1's & 0's Detectors

   - 1's detector: N-input AND gate
- 0's detector: NOTs + 1's detector (N-input NOR)




Equality Comparator

 - Check if each bit is equal (XNOR, aka equality gate)
- 1's detect on bitwise equality



Magnitude Comparator

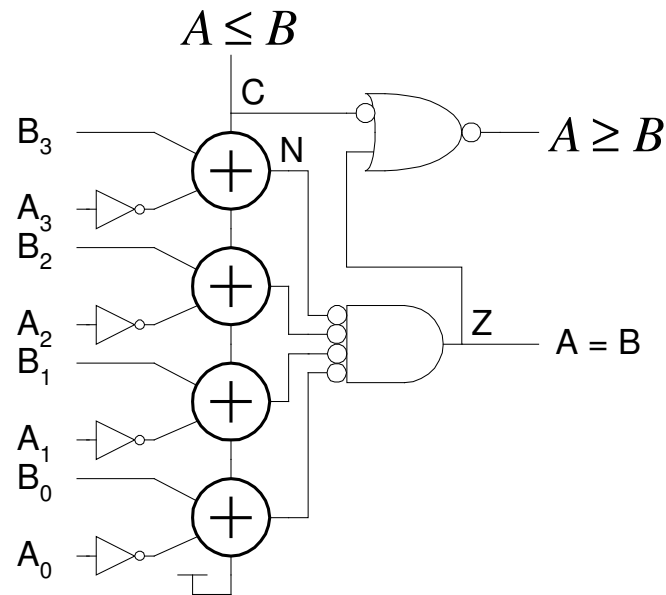
- Compute $B-A$ and look at sign
- $B-A = B + \sim A + 1$
- For unsigned numbers, carry out is sign bit



Shifters

- Logical Shift:
 - Shifts number left or right and fills with 0's
 - 1011 LSR 1 = 0101 1011 LSL1 = 0110
- Arithmetic Shift:
 - Shifts number left or right. Rt shift sign extends
 - 1011 ASR1 = 1101 1011 ASL1 = 0110
- Rotate:
 - Shifts number left or right and fills with lost bits
 - 1011 ROR1 = 1101 1011 ROL1 = 0111


The Binary Shifter

 

Multi-bit Shifters

- Cascade one-bit shifters?
- Complex, unwieldy, slow for larger number of shifts
- Two other types of shifters
 - Barrel shifter
 - Logarithmic shifter


The Barrel Shifter

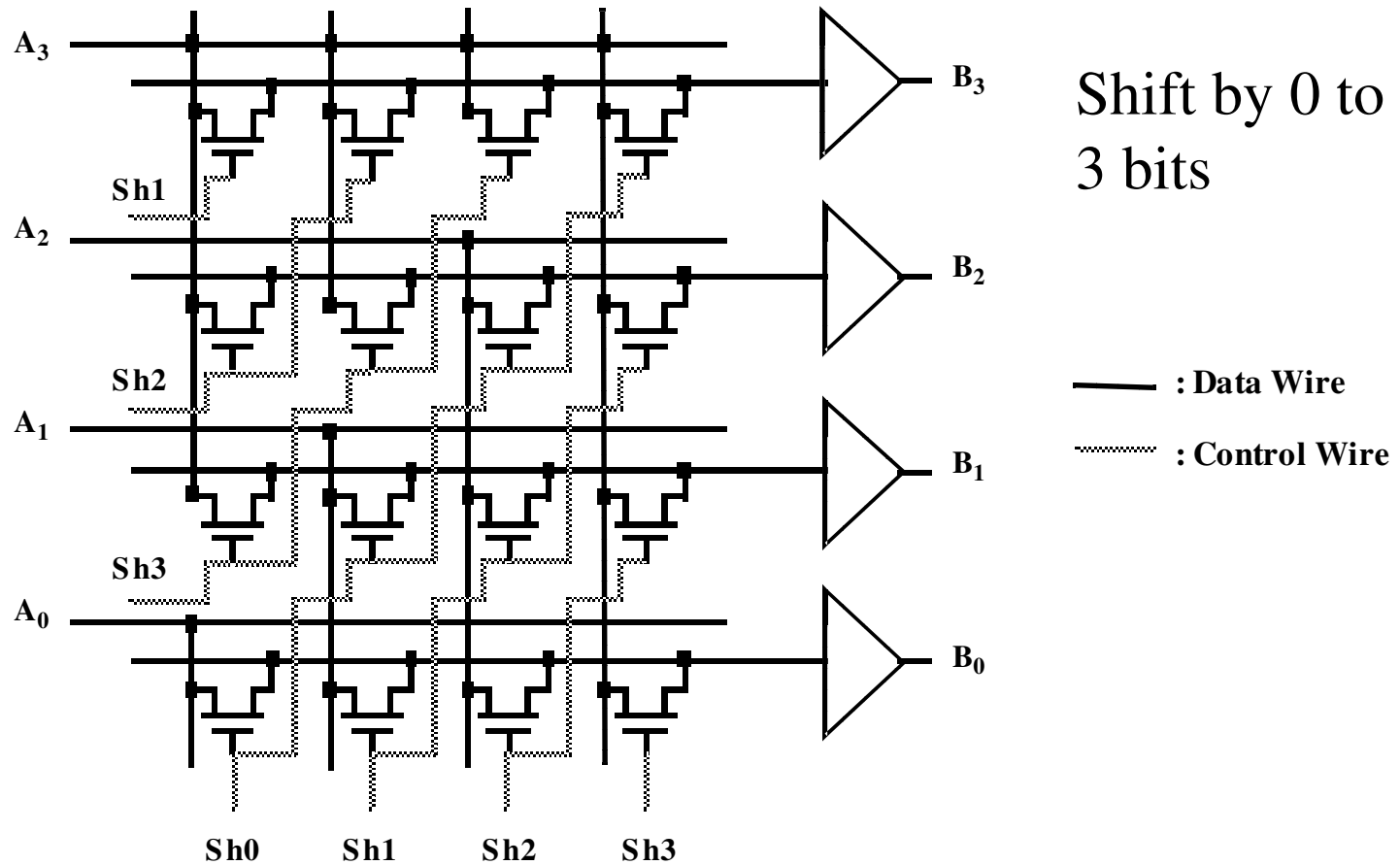

The Barrel Shifter

- Area dominated by wiring
- Propagation delay is theoretically constant (at most one transmission gate), independent of shifter size, no. of shifts
- Reality: Capacitance on buffer input \propto maximum shift width

4x4 barrel shifter

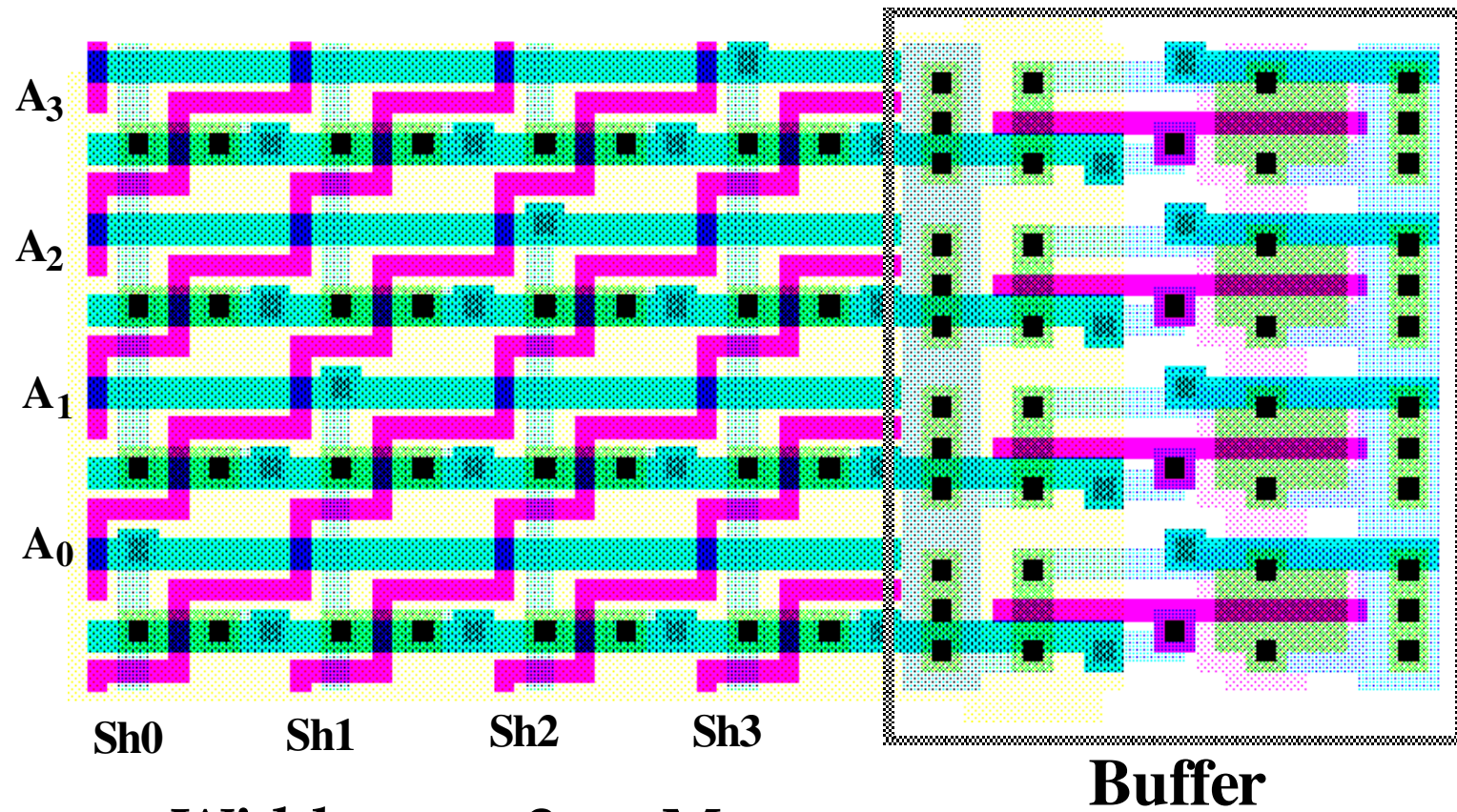


$$\text{Width}_{\text{barrel}} \sim 2 p_m M$$

p_m = metal/poly pitch


M = no. of shifts

Logarithmic Shifter

 - Staged approach, e.g. $7 = 1 + 2 + 4$, $5 = 1 + 0 + 4$
- Shifter with maximum shift width M consists of $\log_2 M$ stages




0-7 bit Logarithmic Shifter

 

$$width_{\log} \approx p_m \left(2K + \left(1 + 2 + \dots + 2^{K-1} \right) \right) = p_m \left(2^K + 2K - 1 \right)$$

Funnel Shifter

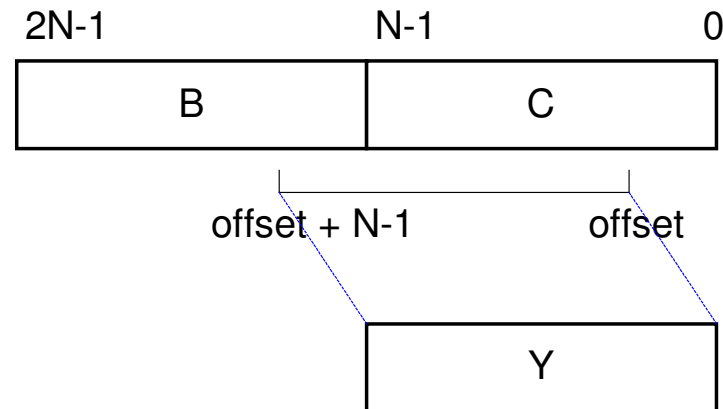- A funnel shifter can do all six types of shifts
- Selects N -bit field Y from $2N$ -bit input
 - Shift by k bits ($0 \leq k < N$)



Funnel Shifter Operation


Table 10.10 Funnel shifter operation

Shift Type	B	C	Offset
Logical Right	$0\dots 0$	$A_{N-1}\dots A_0$	k
Logical Left	$A_{N-1}\dots A_0$	$0\dots 0$	$N-k$
Arithmetic Right	$A_{N-1}\dots A_{N-1}$ (sign extension)	$A_{N-1}\dots A_0$	k
Arithmetic Left	$A_{N-1}\dots A_0$	0	$N-k$
Rotate Right	$A_{N-1}\dots A_0$	$A_{N-1}\dots A_0$	k
Rotate Left	$A_{N-1}\dots A_0$	$A_{N-1}\dots A_0$	$N-k$

- Computing $N-k$ requires an adder

Funnel Shifter Design 1

 - N N-input multiplexers
 - Use 1-of-N hot select signals for shift amount
 - nMOS pass transistor design (V_t drops!)



Funnel Shifter Design 2

- Log N stages of 2-input muxes
 - No select decoding needed

