

# 4-Bit DAC

Matthew Roberts


# Outline

- Abstract
- Schematic
- Output
- Simulation Plan and Results
- Layout
- Final Specifications

# Abstract

- The objective is to design a device that will extract an analog signal given a series of digital codes with the proper time delay.

# Schematic

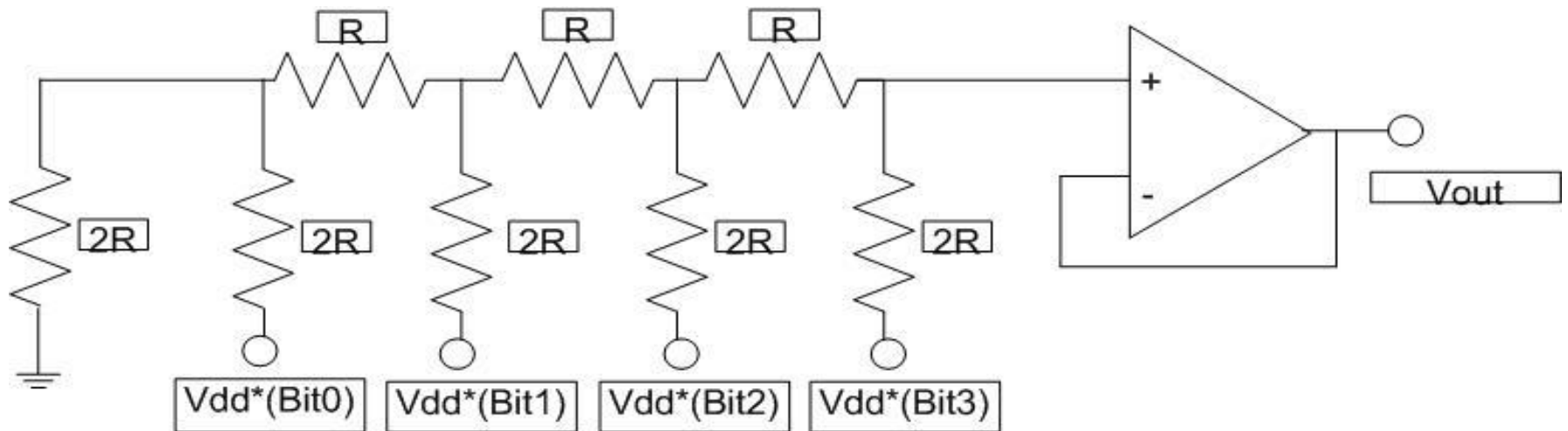


$$V_{out} = \frac{V_{dd}}{2^N} \left( Bit_{N-1} 2^{N-1} + Bit_{N-2} 2^{N-2} + \dots + Bit_0 2^0 \right) = \frac{V_{dd}}{16} \left( 8(Bit_3) + 4(Bit_2) + 2(Bit_1) + Bit_0 \right) =$$

$$V_{dd} \left( \frac{1}{2} Bit_3 + \frac{1}{4} Bit_2 + \frac{1}{8} Bit_1 + \frac{1}{16} Bit_0 \right)$$

$$R = 8k\Omega$$
 
# Output


$$\Delta V = V_{\max} / 2^n = 3.75 / 16 = 0.23V$$




# Simulation Plan

- Test the linearity
- Use pulse sources on each input to run through all possible input combinations
- Generate an approximation of a ramp function.

# Simulation Results - Output

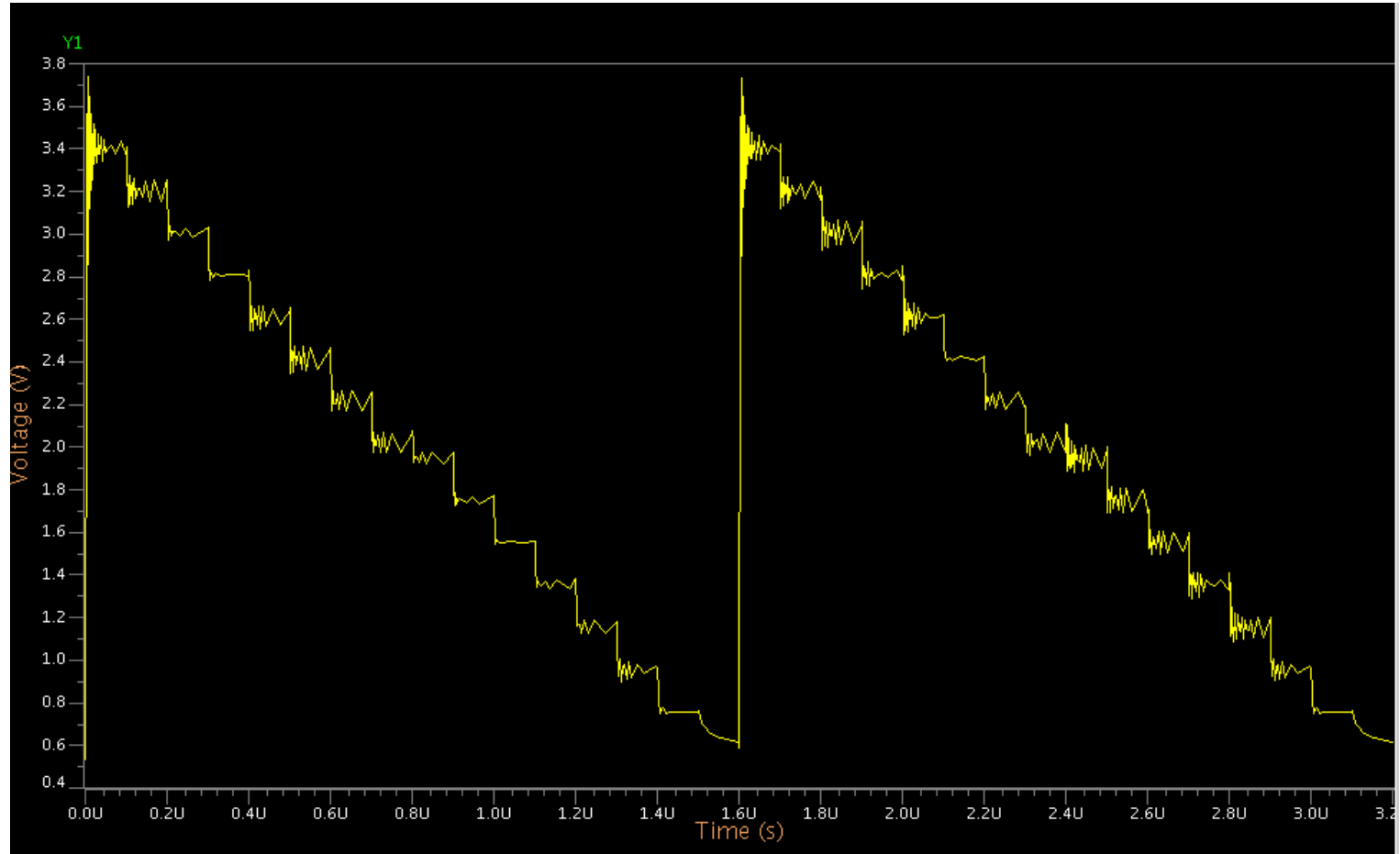


# Overall Schematic

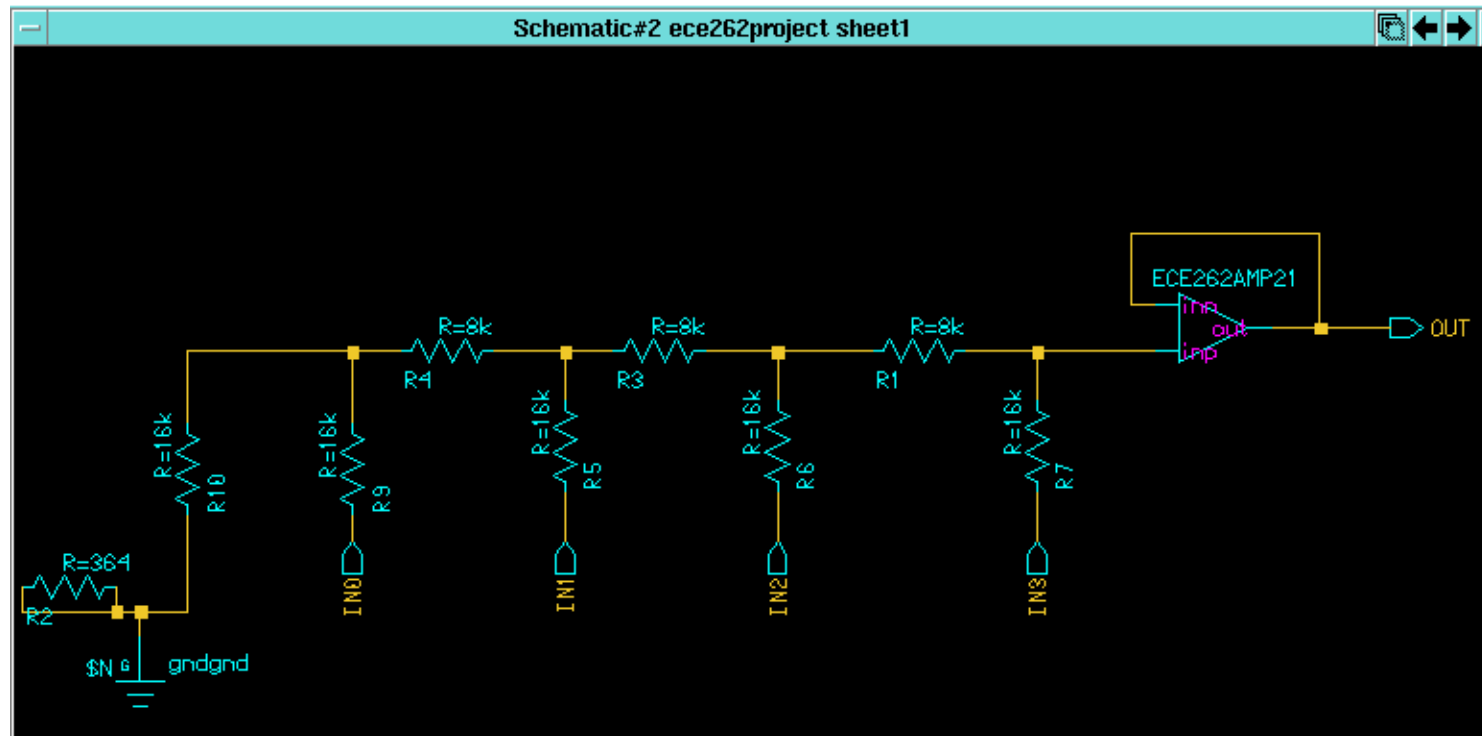




# Op-amp schematic

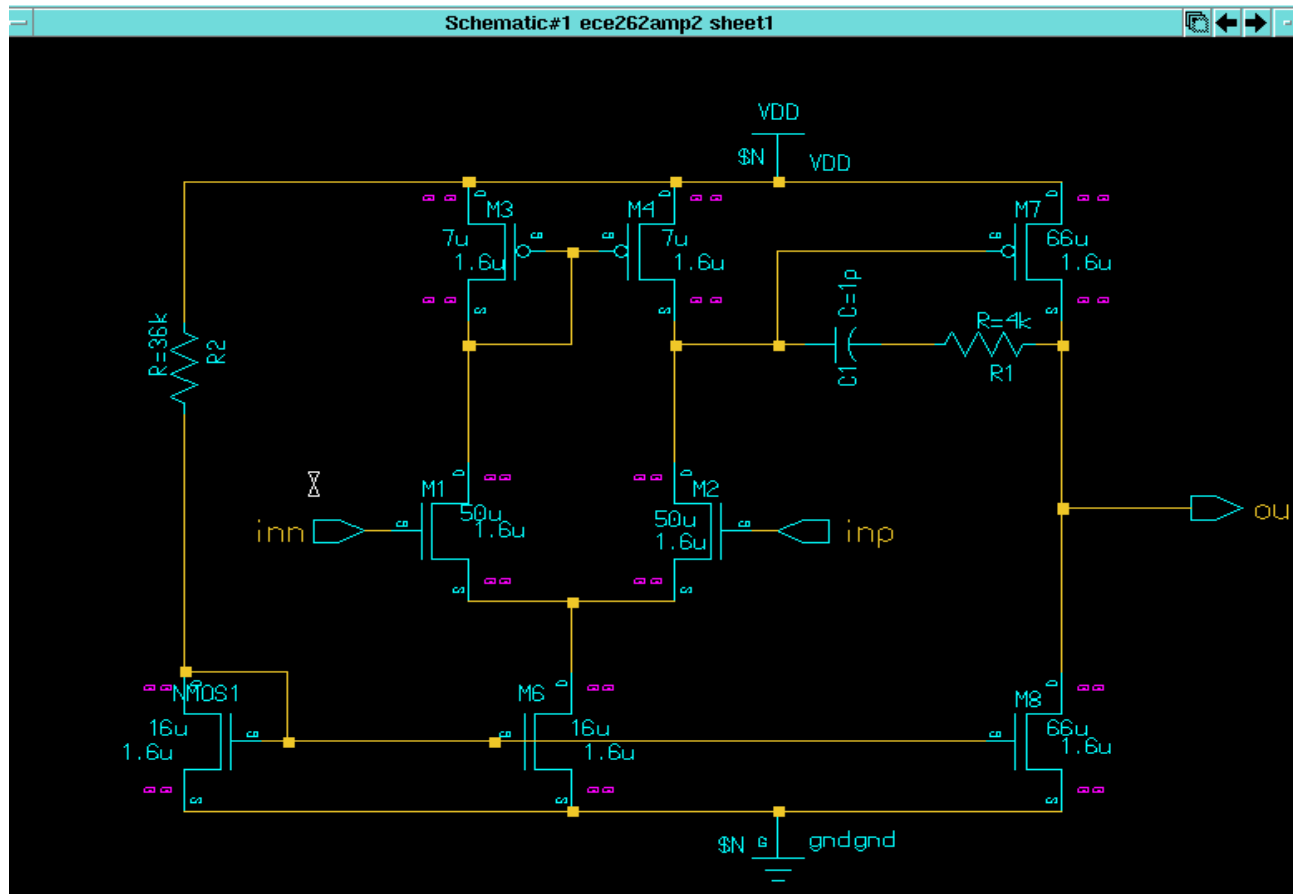

# Layout

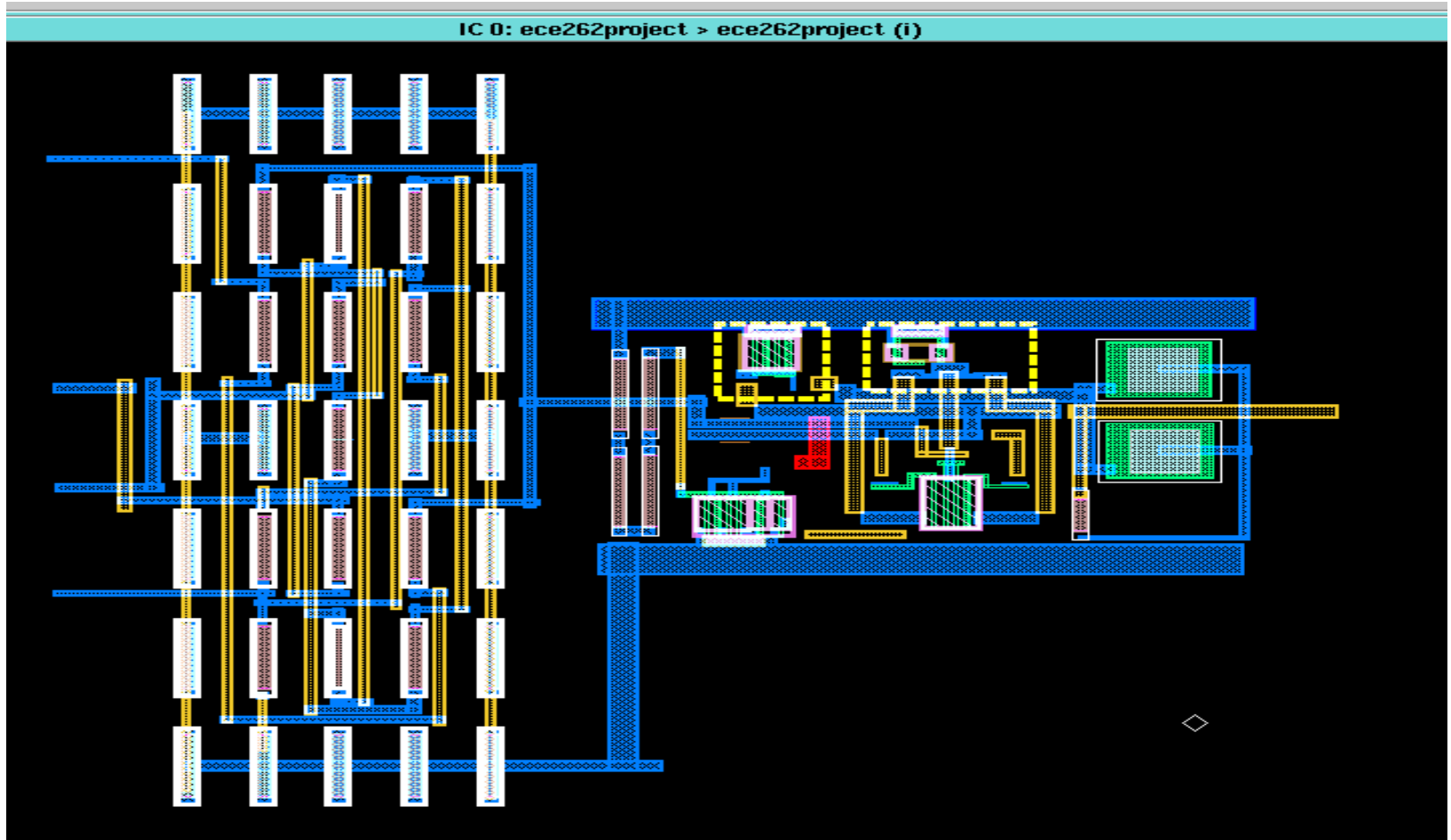

# Final Specifications

- $V_{dd} = 5V$
- Amplifier Power Dissipation =  $5V \times 0.6mA = 3mW$
- Resistor power dissipation (WC) –  
 $(5V)^2 / 24k\Omega = 1mW$
- Total Power Dissipation – **4mW**
- For the output stage: The following spec was met

$$\Delta t < \frac{T_{min}}{2^{N+1}}; \frac{\Delta V}{SR} = \frac{V_{dd}}{2^N SR} < \frac{1}{f_{max} 2^{N+1}}; \frac{V_{dd}}{SR} < \frac{1}{2f_{max}}; SR > 2V_{dd} f_{max} = 2 \times 5V \times 100MHz$$

$$SR > 1 \frac{mV}{ps}$$

# Final Specifications (cont.)

- Components
  - 5 resistors with resistance  $2R$
  - 3 resistors with resistance  $R$
  - Op-amp
    - 8 transistors
    - 2 resistors
    - 1 capacitor
- Unit Resistance ( $R$ ) =  $8\text{k}\Omega$ 
  - $2R = 16\text{k}\Omega$
- Area of layout =  $390\mu\text{m} \times 458\mu\text{m} = 178,620(\mu\text{m})^2 = 0.18(\text{mm})^2$

# Design Challenges

- The biggest design challenge was figuring out some LVS problems with device models.
- It was also a challenge to modify an existing op-amp layout to suit my purposes and to hook up a large number of resistors in a common-centroid layout.
- The rest of the design process went very smoothly